




Design Of A Mini Data Path

Part 1

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)


Data Paths and Control

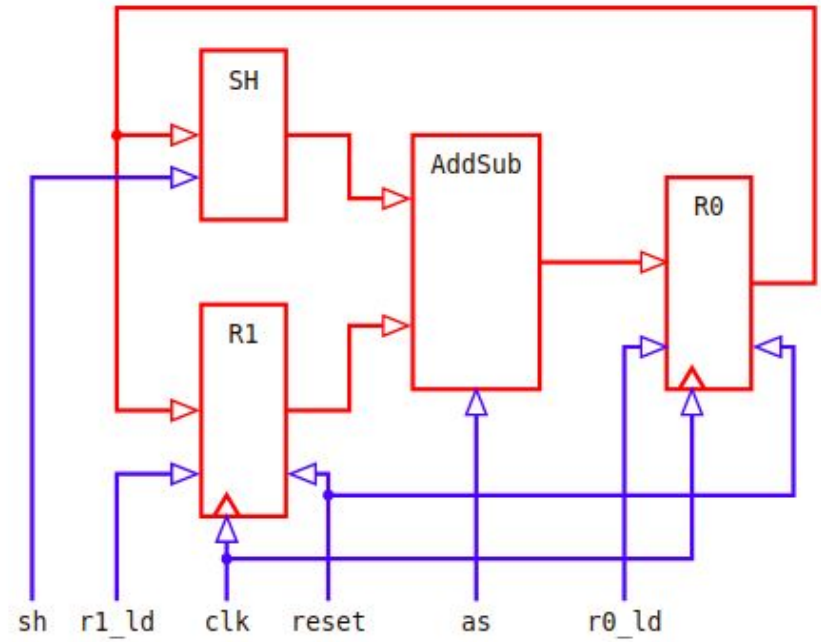- A data path consists of registers, adders, subtractors, shifters, and any circuit that modifies a data value
- The design of most computers consist of a data path and control logic.
- A finite state machine (FSM) is used to control the operations of the data path
 - Part 2




Data Paths and Control

 - The blue lines are part of the control logic
- The red lines are part of the data path



Data Paths and Control

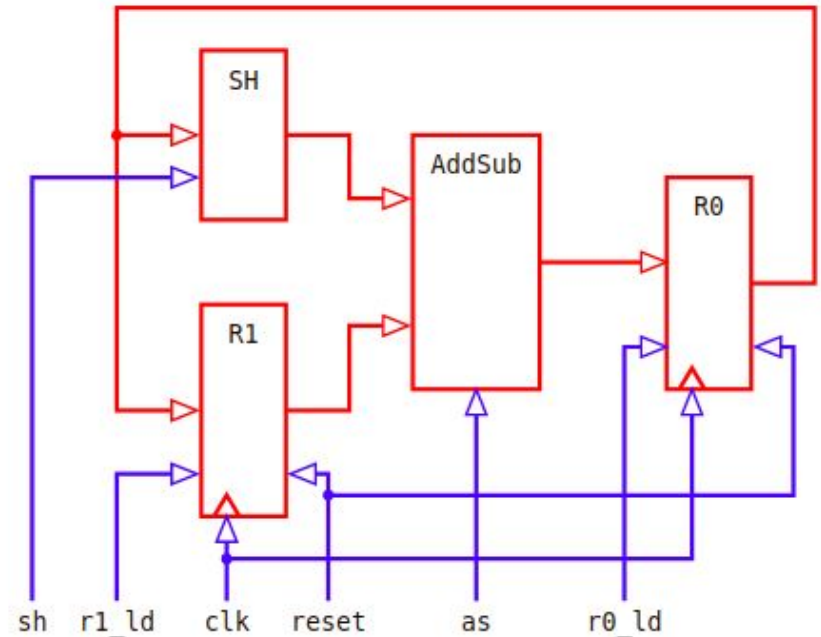
- Data path contains:
 - Add/subtract module
 - Two 16-bit registers (R1 and R0)
 - Combinational logic block (SH) to generate:
 - 1
 - -1
 - multiply by 2
 - pass through R0
- These modules can be used to generate integer sequences



Load and Reset Register

- On the positive edge:
 - If reset is 1: register is set to all zeros
 - If the ld input is 1: register is loaded from the data inputs.
 - If reset and ld are both 0: the register is not changed.
- R1 and R0 works the same way
- 16-bit type definition:

```
typedef logic [15:0] reg16_t;
```

 

Load and Reset Register

ld_reg.v



- On the positive edge:
 - If reset is 1: register is set to all zeros
 - If the ld input is 1: register is loaded from the data inputs.
 - If reset and ld are both 0: the register is not changed.
- R1 and R0 works the same way
- 16-bit type definition:

```
typedef logic [15:0] reg16_t;
```

```
module ld_reg(output reg16_t q,  
              input reg16_t d,  
              input logic clk, reset, ld);  
  
    always_ff @(posedge clk) begin  
        if ( reset ) begin q <= 0; end  
        else begin if ( ld ) q <= d; end  
    end  
  
endmodule
```

Add/Subtract Module

  - Module “as_alu”
 - output: out
 - input: a, b, ctl
- The out data is either:
 - $a + b$
 - $a - b$
 - a
 - b
- Depends on the control input
- ALU will be more complex
- ALU symbol
 - O: operation
 - S: flags (CNZV)
 - A, B: Operands
 - X: Result



Add/Subtract Module

- The out data is either:
 - $a + b$ // AS_ADD
 - $a - b$ // AS_SUB
 - a // AS_a
 - b // AS_b
- Depending on the control input
- `as_ctl_t` is an enumeration of all operations

```
typedef enum logic [1:0] { AS_ADD, AS_SUB, AS_A, AS_B } as_ctl_t;
```


Add/Subtract Module

as_alu.v


- The out data is either:
 - $a + b$ // AS_ADD
 - $a - b$ // AS_SUB
 - a // AS_A
 - b // AS_B
- Depending on the control input
- as_ctl_t is an enumeration of all operations

```
typedef enum logic [1:0] {  
    AS_ADD,  
    AS_SUB,  
    AS_A,  
    AS_B } as_ctl_t;
```

```
always_comb begin  
    case( ctl )  
        AS_ADD : out = a + b;  
        AS_SUB : out = a - b;  
        AS_A   : out = a;  
        AS_B   : out = b;  
    endcase  
end
```

Shifter Module

 - Operand “a” for the Add/Sub
- Recover the value of R0
- The shifter module
 - a. passes its input to the output
 - b. shifts the input one position to the left ($r0 * 2$)
 - c. provides a constant 1
 - d. provides a constant all ones
- All ones is -1 (two's complement)



Shifter Module

- The shifter module
 - passes its input to the output
 - shifts the input one position to the left ($r0 * 2$)
 - provides a constant 1
 - provides a constant all ones
- In two's complement, all ones is -1.
- `shift_ctl_t` is the enumeration for the operations of the shifter module.

```
typedef enum logic [1:0] {SH_PASS,SH_LEFT,SH_ONE,SH_ONES} shift_ctl_t;
```

Shifter Module

shifter.v


- The shifter module
 - passes its input to the output
 - shifts the input one position to the left ($r0 * 2$)
 - provides a constant 1
 - provides a constant all ones
- In two's complement, all ones is -1.
- shift_ctl_t is the enumeration for the operations of the shifter module.

```
typedef enum logic [1:0] {SH_PASS, SH_LEFT,  
SH_ONE, SH_ONES} shift_ctl_t;
```

```
always_comb begin  
  
    case( ctl )  
  
        SH_PASS: out = in;  
  
        SH_LEFT: out = in << 1;  
  
        SH_ONE: out = 1;  
  
        SH_ONES: out = 16'hffff;  
  
    endcase  
  
end
```


Data Paths and Control in Verilog

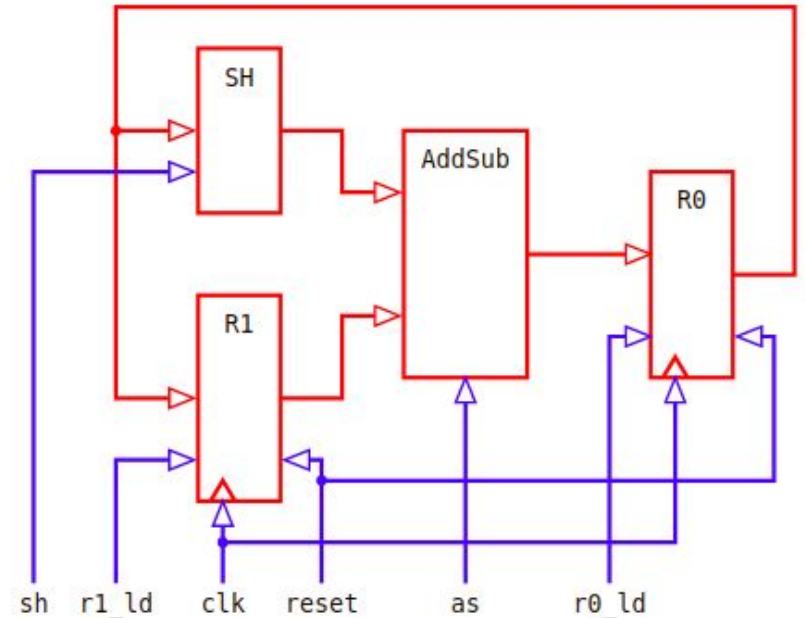- Putting everything together
- Sequence generator module (seq_gen_dp.v)
- output
 - reg16_t out
- input
 - clk
 - reset
 - as_ctl
 - shift_ctl
 - r1_ld
 - r0_ld



Data Paths and Control in Verilog

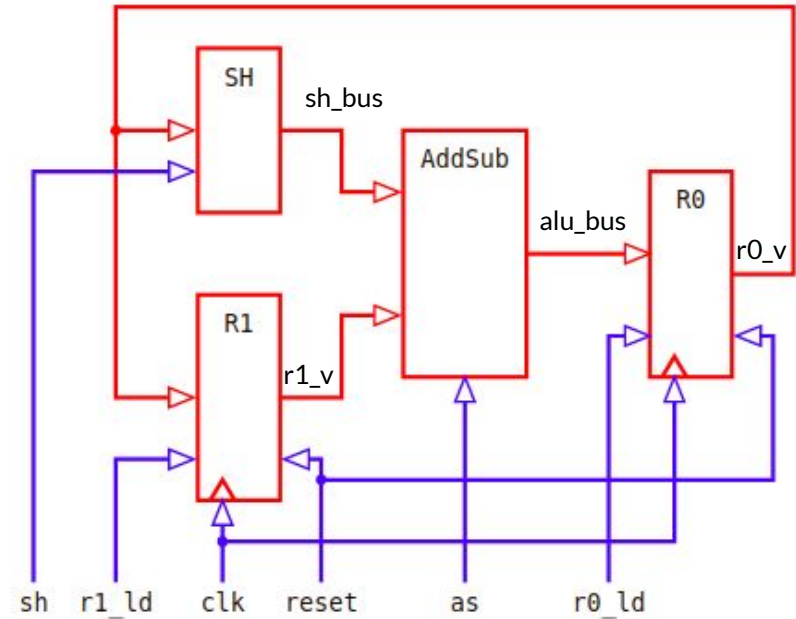
- Putting everything together
- Sequence generator module (seq_gen_dp.v)
- Busses:
 - alu_bus
 - sh_bus
 - r0_v
 - r1_v



Data Paths and Control in Verilog

- Putting everything together
- Sequence generator module (seq_gen_dp.v)

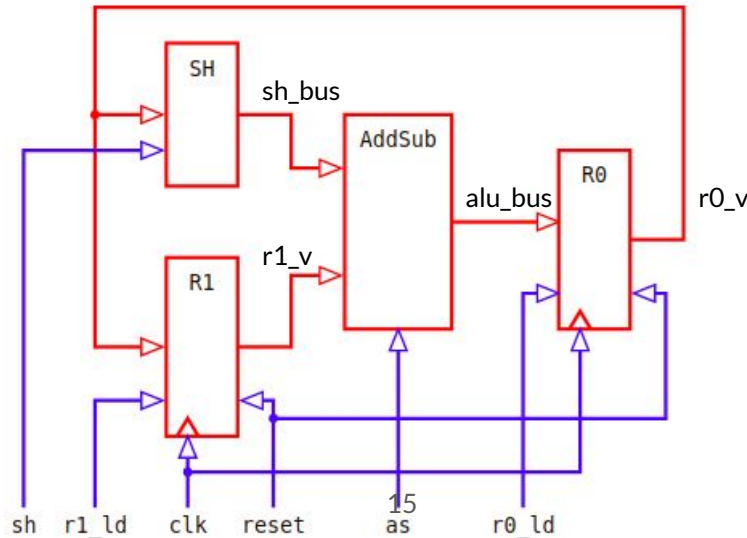
```
shifter SH( .out(sh_bus), .in(r0_v), .ctl(shift_ctl) );
```



Data Paths and Control in Verilog

- Putting everything together
- Sequence generator module (seq_gen_dp.v)

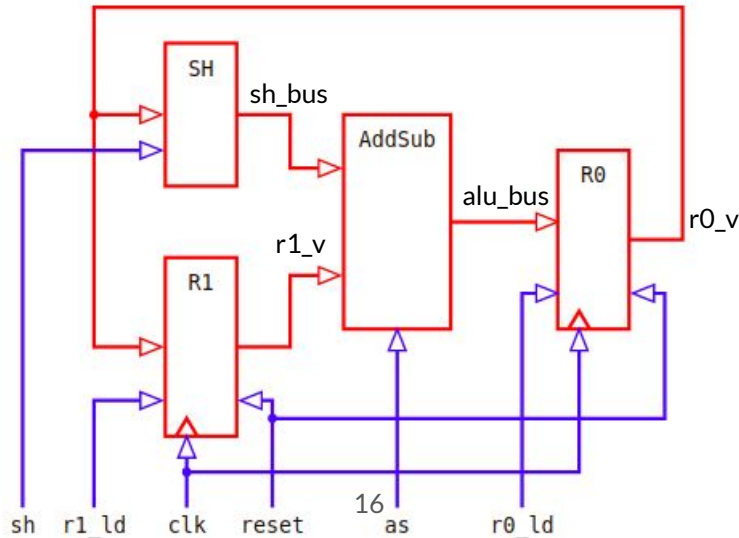
```
ld_reg R1(.q(r1_v), .d(r0_v), .clk(clk), .reset(reset), .ld(r1_ld));
```



Data Paths and Control in Verilog

- Putting everything together
- Sequence generator module (seq_gen_dp.v)

 
```
as_alu ALU( .out(alu_bus), .a(sh_bus), .b(r1_v), .ctl(as_ctl) );
```



Data Paths and Control in Verilog


- Putting everything together
- Sequence generator module (seq_gen_dp.v)
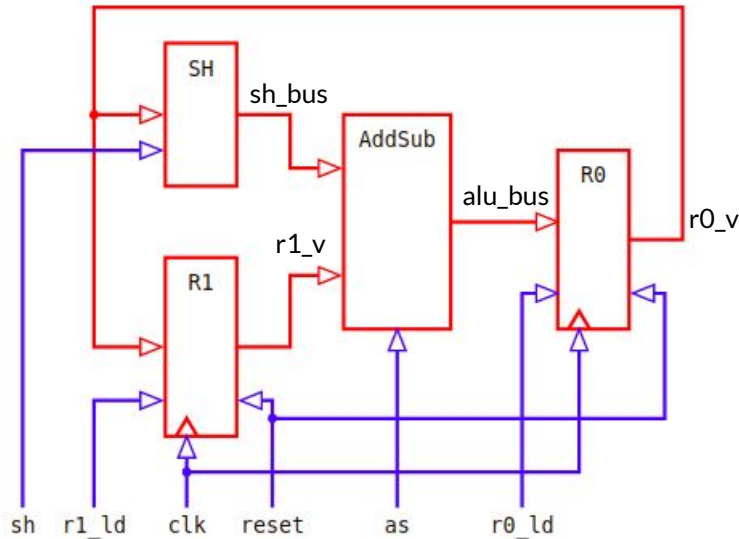
```
ld_reg R0( .q(r0_v), .d(alu_bus), .clk(clk), .reset(reset), .ld(r0_ld) );
```



Data Paths and Control in Verilog

 
- Putting everything together
- Sequence generator module (seq_gen_dp.v)
- iverilog -g2012 tb_rtl.v
 - $R0 \leq 1$
 - $R1 \leq R0$



Data Paths and Control in Verilog

- Putting everything together
- Sequence generator module (seq_gen_dp.v)

```
assign out = r0_v;
```

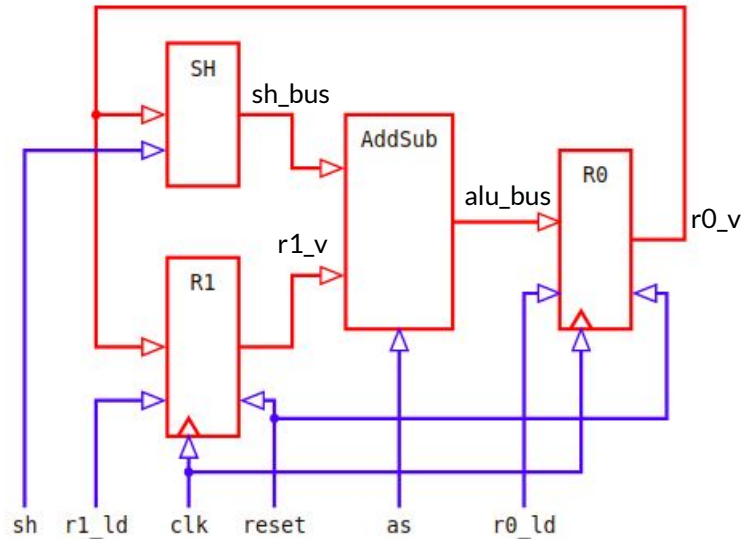

End of part 1

- Design of a mini data path
- Next part:
 - Test the mini datapath
 - Register Transfer Level (RTL) Design