



# Boolean Algebra

Instructor: Dr. Vinicius Prado da Fonseca ([vpradodafons@online.mun.ca](mailto:vpradodafons@online.mun.ca))

# Boolean Algebra Introduction

---

- Modern digital systems use 0 and 1 to describe values and boolean equations to describe behaviours.
- Algebra to simplify arithmetic equations
- Boolean algebra to simplify Boolean equations.
- Rules Boolean algebra are much like those of ordinary algebra
- In some cases simpler, because variables have only two possible values: 0 or 1.

# Boolean Algebra Introduction - Axioms

- Boolean algebra is based on a set of axioms we assume are correct.
- Axioms are unprovable.
- Set of definitions.
- From these axioms, we prove all the theorems of Boolean algebra.

NOT  
 $\bar{a}$

a	x
0	1
1	0

AND  
 $a \cdot b$

a	b	x
0	0	0
0	1	0
1	0	0
1	1	1

OR  
 $a + b$

a	b	x
0	0	0
0	1	1
1	0	1
1	1	1

# Boolean Algebra Introduction - Axioms

- Duality of Boolean Algebra.
- AND and OR are duals of each other.

NOT

$$\overline{0} = 1 \text{ and } \overline{1} = 0$$

AND

$$0 \cdot 0 = 0, 0 \cdot 1 = 0, 1 \cdot 0 = 0, \text{ and } 1 \cdot 1 = 1,$$

OR

$$0 + 0 = 0, 0 + 1 = 1, 1 + 0 = 1, \text{ and } 1 + 1 = 1,$$

NOT $\overline{a}$	
a	x
0	1
1	0

AND $a \cdot b$		
a	b	x
0	0	0
0	1	0
1	0	0
1	1	1

OR $a + b$		
a	b	x
0	0	0
0	1	1
1	0	1
1	1	1

# Boolean Algebra Introduction - Axioms

- Duality of Boolean Algebra
- AND and OR are duals of each other

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

# Single Variable Boolean Algebra Theorems

- Identity for AND

$$a \cdot 1 = a$$

- Identity for OR

$$a + 0 = a$$

- Annihilator for AND

$$a \cdot 0 = 0$$

- Annihilator for OR

$$a + 1 = 1$$



a	1	$a \cdot 1$
0	1	0
1	1	1

# Single Variable Boolean Algebra Theorems

- Identity for AND

$$a \cdot 1 = a$$

- Identity for OR


$$a + 0 = a$$

- Annihilator for AND

$$a \cdot 0 = 0$$

- Annihilator for OR

$$a + 1 = 1$$

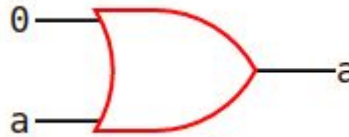

<b>a</b>	<b>0</b>	<b>a + 0</b>
0	0	0
1	0	1

# Single Variable Boolean Algebra Theorems

- Identity for AND

$$a \cdot 1 = a$$

- Identity for OR


$$a + 0 = a$$

- Annihilator for AND

$$a \cdot 0 = 0$$

- Annihilator for OR

$$a + 1 = 1$$

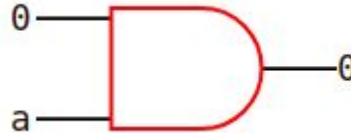

<b>a</b>	<b>0</b>	<b><math>a \cdot 0</math></b>
0	0	0
1	0	0



# Single Variable Boolean Algebra Theorems

- Identity for AND

$$a \cdot 1 = a$$

- Identity for OR

$$a + 0 = a$$


- Annihilator for AND

$$a \cdot 0 = 0$$

- Annihilator for OR

$$a + 1 = 1$$

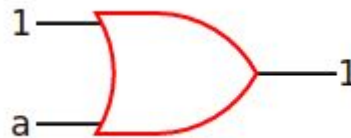You may want to test all these properties for longer values of input  $a$  (e.g.,  $a = 100101$ )




<b>a</b>	<b>1</b>	<b>a + 1</b>
0	1	1
1	1	1

# Single Variable Boolean Algebra Theorems

- Idempotent law (**no change**) for AND and OR

$$a \cdot a = a$$

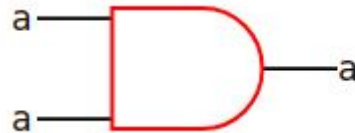

<b>a</b>	<b>a</b>	<b><math>a \cdot a</math></b>
0	0	0
1	1	1

$$a + a = a$$



<b>a</b>	<b>a</b>	<b><math>a + a</math></b>
0	0	0
1	1	1

# Single Variable Boolean Algebra Theorems

- Complement for AND and OR

$$a \cdot \bar{a} = 0$$



<b>a</b>	<b><math>\bar{a}</math></b>	<b><math>a \cdot \bar{a}</math></b>
0	1	0
1	0	0

$$a + \bar{a} = 1$$



<b>a</b>	<b><math>\bar{a}</math></b>	<b><math>a + \bar{a}</math></b>
0	1	1
1	0	1

# Single Variable Boolean Algebra Theorems

- Involution (double NOT)

$$\overline{\overline{a}} = a$$

- “Double negation” cancel each other
  - Not over operators (DeMorgan's):

$$\overline{\overline{A + B}} \neq A + B$$

# Multi variable Theorems

- Commutativity of AND

$$a \cdot b = b \cdot a$$

- Commutativity of OR

$$a + b = b + a$$

- Associativity of AND

$$(a \cdot b) \cdot c = a \cdot (b \cdot c)$$

- Associativity of OR

$$(a + b) + c = a + (b + c)$$

# Boolean Algebra Theorems

- Distributivity of AND over OR

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

The operation inside goes to outside

a	b	c	b+c	a(b+c)	a	b	c	ab	ac	ab+ac
0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0
0	1	0	1	0	0	1	0	0	0	0
0	1	1	1	0	0	1	1	0	0	0
1	0	0	0	0	1	0	0	0	0	0
1	0	1	1	1	1	0	1	0	1	1
1	1	0	1	1	1	1	0	1	0	1
1	1	1	1	1	1	1	1	1	1	1

# Boolean Algebra Theorems

- Distributivity of OR over AND

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

The operation inside goes to outside

a	b	c	bc	a+bc	a	b	c	a+b	a+c	x
0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	0	1	0
0	1	0	0	0	0	1	0	1	0	0
0	1	1	1	1	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	1
1	0	1	0	1	1	0	1	1	1	1
1	1	0	0	1	1	1	0	1	1	1
1	1	1	1	1	1	1	1	1	1	1

# More Simplification Boolean Algebra Theorems

Covering (Absorption) of AND and OR (Truth tables)

- $a \cdot (a + b) = a$ 
  - $0 \cdot (0 + b) = 0$  (annihilator of AND)
  - $1 \cdot (1 + b) = 1$  (annihilator of OR)
- $a + (a \cdot b) = a$  (Same truth table as above, simplification turns this on the other)

Combining of AND and OR

- $(a \cdot b) + (a \cdot \bar{b}) = a \cdot (b + \bar{b}) = a \cdot 1 = a$
- $(a + b) \cdot (a + \bar{b}) = a + (b \cdot \bar{b}) = a + 0 = a$



# More Simplification Boolean Algebra Theorems

- Consensus (Redundancy)
  - The consensus or resolvent of the terms  $AB$  and  $A'C$  is  $BC$
  - It is the conjunction of all the unique literals of the terms
  - excluding the literal that appears unnegated in one term and negated in the other.
- $(AB) + (\bar{A}C) + (BC) = AB + \bar{A}C$
- $(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$


# More Simplification Boolean Algebra Theorems

- DeMorgan's Law
- Invert the operations and invert literals


$$\overline{a \cdot b} = \overline{a} + \overline{b}$$
$$\overline{a + b} = \overline{a} \cdot \overline{b}$$



is equivalent to

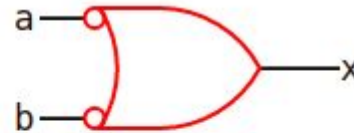

is equivalent to

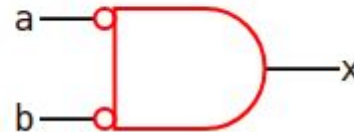

# Sum of Products

How to write a Boolean equation for any logic function given its truth table.


OR

SOP	A	B	x
$\overline{A} \cdot \overline{B}$	0	0	0
$\overline{A} \cdot B$	0	1	1
$A \cdot \overline{B}$	1	0	1
$A \cdot B$	1	1	1
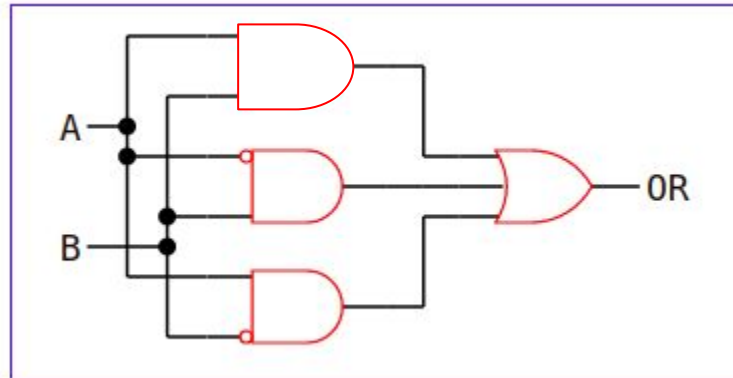
# Sum of Products

How to write a Boolean equation for any logic function given its truth table.

$$\overline{A} \cdot B + A \cdot \overline{B} + A \cdot B$$




OR

SOP	A	B	x
$\overline{A} \cdot \overline{B}$	0	0	0
$\overline{A} \cdot B$	0	1	1
$A \cdot \overline{B}$	1	0	1
$A \cdot B$	1	1	1
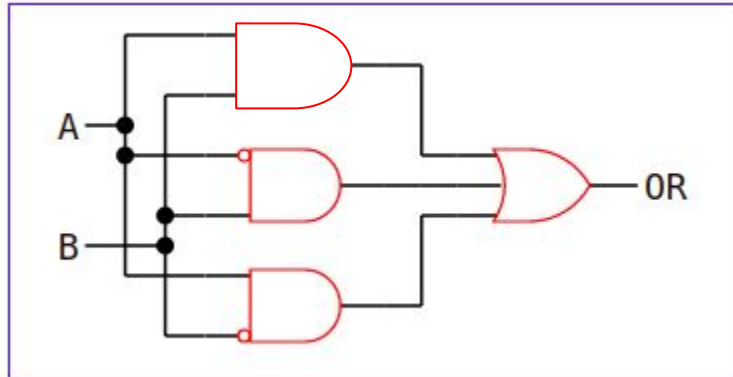
# Sum of Products

- Boolean expression contain AND, OR, and NOT operators
- The Canonical form contain all the variables, ANDed. Products are ORed together
- Any Boolean function can be described using a SOP expression
- Non minimal form/canonical form

$$\overline{A} \cdot B + A \cdot \overline{B} + A \cdot B$$



OR

SOP	A	B	x
$\overline{A} \cdot \overline{B}$	0	0	0
$\overline{A} \cdot B$	0	1	1
$A \cdot \overline{B}$	1	0	1
$A \cdot B$	1	1	1

# Minterms

- A truth-table can be specified by listing its minterms that are true
- Equivalent to a SOP expression
- Function  $f$  has minterms
  - $m_3, m_5, m_6, m_7$

$\Sigma(m_3, m_5, m_6, m_7)$  or  $\Sigma(3, 5, 6, 7)$

Minterms	SOP	A	B	C	f
$m_0$	$\overline{A} \cdot \overline{B} \cdot \overline{C}$	0	0	0	0
$m_1$	$\overline{A} \cdot \overline{B} \cdot C$	0	0	1	0
$m_2$	$\overline{A} \cdot B \cdot \overline{C}$	0	1	0	0
$m_3$	$\overline{A} \cdot B \cdot C$	0	1	1	1
$m_4$	$A \cdot \overline{B} \cdot \overline{C}$	1	0	0	0
$m_5$	$A \cdot \overline{B} \cdot C$	1	0	1	1
$m_6$	$A \cdot B \cdot \overline{C}$	1	1	0	1
$m_7$	$A \cdot B \cdot C$	1	1	1	1

# Product of Sums

- Boolean expression contain AND, OR, and NOT operators
- ANDed (product) a collection of OR terms (sum)


AND

POS	A	B	x
$(A + B)$	0	0	0
$(A + \overline{B})$	0	1	0
$(\overline{A} + B)$	1	0	0
$(\overline{A} + \overline{B})$	1	1	1
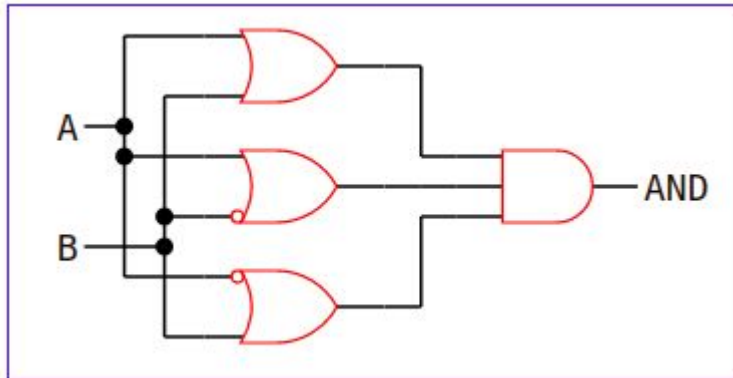
# Product of Sums

- Boolean expression contain AND, OR, and NOT operators
- ANDed (product) a collection of OR terms (sum)

$$(A + B) \cdot (A + \overline{B}) \cdot (\overline{A} + B)$$



AND

POS	A	B	x
$(A + B)$	0	0	0
$(A + \overline{B})$	0	1	0
$(\overline{A} + B)$	1	0	0
$(\overline{A} + \overline{B})$	1	1	1



# Maxterms

- A truth-table can be specified by listing its maxterms that are false
- equivalent to a POS expression
- Function  $f$  has maxterms
  - $M_1, M_2$

$\prod(m_1, m_2)$  or  $\prod(1, 2)$

Maxterms	POS	A	B	f
$M_0$	$(A + B)$	0	0	1
$M_1$	$(A + \overline{B})$	0	1	0
$M_2$	$(\overline{A} + B)$	1	0	0
$M_3$	$(\overline{A} + \overline{B})$	1	1	1

# Boolean expressions to truth tables

$$F = ((\sim b \ \& \ \sim a) \mid (b \ \& \ a))$$

<b>a</b>	<b>b</b>	<b>F</b>
0	0	
0	1	
1	0	
1	1	

# Boolean expressions to truth tables

$$F = ((\sim b \ \& \ \sim a) \mid (b \ \& \ a))$$

<b>a</b>	<b>b</b>	<b>F</b>
0	0	1
0	1	0
1	0	0
1	1	1

# Boolean expressions to truth tables

$$F = ((\sim a \ \& \ c) \mid (b \ \& \ a \ \& \ \sim c) \mid (\sim b \ \& \ c) \mid (\sim b \ \& \ \sim a))$$

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Boolean expressions to truth tables

$$F = ((\sim a \ \& \ c) \mid (b \ \& \ a \ \& \ \sim c) \mid (\sim b \ \& \ c) \mid (\sim b \ \& \ \sim a))$$

a	b	c	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

# Simplification examples

---

- Extra video lecture



# Questions?

- Next class
- K-Maps
- Simplification of boolean expressions