



K-Maps

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Karnaugh Maps Definitions

- Boolean algebra is prone to errors, requires memorization of rules and theorems
- Karnaugh Maps are a graphical method for simplifying boolean equations
- Invented in 1953 by Maurice Karnaugh

Karnaugh Maps Definitions

- Logic minimization involves combining terms (Minterms, SOP)
- Two terms containing an implicant P and the true and complementary forms of some variable A are combined to eliminate A:

$$PA + P\bar{A} = P$$

Eliminating redundant terms:

Ex: Minterms 3, 7 = $\bar{a}bc$, abc

If the function is true in both cases ($F = \bar{a}bc + abc$) with “ $\sim a$ ” or “ a ”, so it doesn't matter, we can eliminate the literal “ a ” and keep only “ bc ”.

Karnaugh Maps Definitions

- Two dimensional truth table for 2, 3, and 4 variable functions
- There also 5 and 6 variable K-maps. Not covered.

a	b	x
0	0	0
0	1	0
1	0	0
1	1	1

A AND B

	0	1
0	0	0
1	0	1

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1

A OR B

	0	1
0	0	1
1	1	1

a	b	x
0	0	0
0	1	1
1	0	1
1	1	0

A XOR B

	0	1
0	0	1
1	1	0

Karnaugh Maps Definitions

$$\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

- 3-variable K-map
- K-maps are arranged such that adjacent cell differ by only **one** change
- BC -> 00 | 01 | 11 | 10
- 01 -> 10 (both digits change)
- 01 -> 11 (only first digit change)
- **Numbering the cells helps**

SOP	A	B	C	x
$\overline{A} \cdot \overline{B} \cdot \overline{C}$	0	0	0	0
$\overline{A} \cdot \overline{B} \cdot C$	0	0	1	0
$\overline{A} \cdot B \cdot \overline{C}$	0	1	0	0
$\overline{A} \cdot B \cdot C$	0	1	1	1
$A \cdot \overline{B} \cdot \overline{C}$	1	0	0	0
$A \cdot \overline{B} \cdot C$	1	0	1	1
$A \cdot B \cdot \overline{C}$	1	1	0	1
$A \cdot B \cdot C$	1	1	1	1

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

Karnaugh Maps Definitions

- 4 variable K-Map
- Any adjacent cell also only be different by a change in only one variable
- AB -> 00 | 01 | 11 | 10
- CD -> 00 | 01 | 11 | 10

		cd			
		00	01	11	10
ab	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

Karnaugh Maps For Simplification

$$a \cdot b + a \cdot \bar{b} = a$$

Karnaugh Maps For Simplification

$$a \cdot b + a \cdot \bar{b} = a$$

SOP	a	b	x
$\bar{a} \cdot \bar{b}$	0	0	0
$\bar{a} \cdot b$	0	1	0
$a \cdot \bar{b}$	1	0	1
$a \cdot b$	1	1	1

	b	
	0	1
a	0	0
1	1	1

	b	
	0	1
a	0	0
1	1	1

Two Variable K-map Examples

- Grouping of powers of two implicants
- 1, 2 or 4 implicants
- What is the biggest group I can form with this minterm?

$$\text{NAND } \overline{A} \cdot \overline{B} + \overline{A} \cdot B + A \cdot \overline{B}$$

a	b	x
0	0	1
0	1	1
1	0	1
1	1	0

A NAND B

	B	
	0	1
A	0	1
	1	0

A NAND B

	B	
	0	1
A	0	1
	1	0

A NAND B

	B	
	0	1
A	0	1
	1	0

Karnaugh Maps For Simplification

$$\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC =$$

Karnaugh Maps For Simplification

$$\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC = \mathbf{A \cdot B + A \cdot C + B \cdot C}$$

BC

	00	01	11	10
A 0	0	0	1	0
A 1	0	1	1	1

BC

	00	01	11	10
A 0	0	0	1	0
A 1	0	1	1	1

K-map And Truth Table For Three Variables

- Grouping of powers of two implicants
- 1, 2, 4 or 8 implicants
- What is the biggest group I can form with this minterm?

		BC			
		00	01	11	10
A	0	m0	m1	m3	m2
	1	m4	m5	m7	m6

- m0 is $\overline{A} \cdot \overline{B} \cdot \overline{C}$
- m1 is $\overline{A} \cdot \overline{B} \cdot C$
- m2 is $\overline{A} \cdot B \cdot \overline{C}$
- m3 is $\overline{A} \cdot B \cdot C$
- m4 is $A \cdot \overline{B} \cdot \overline{C}$
- m5 is $A \cdot \overline{B} \cdot C$
- m6 is $A \cdot B \cdot \overline{C}$
- m7 is $A \cdot B \cdot C$

A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	0	0	0	1

Karnaugh Maps For Simplification

$$\begin{aligned} &\sim A \sim B \sim C \sim D + \sim A B \sim C \sim D + A B \sim C \sim D + A \sim B \sim C \sim D + \\ &\sim A \sim B \sim C D + \sim A \sim B C D + \sim A \sim B C \sim D = \end{aligned}$$

Karnaugh Maps For Simplification

$$\begin{aligned} &\sim A \sim B \sim C \sim D + \sim A B \sim C \sim D + A B \sim C \sim D + A \sim B \sim C \sim D + \\ &\sim A \sim B \sim C D + \sim A \sim B C D + \sim A \sim B C \sim D \\ &= \sim A \sim B + \sim C \sim D \end{aligned}$$

CD

	00	01	11	10
00	1	1	1	1
01	1	0	0	0
11	1	0	0	0
10	1	0	0	0

AB

Four Variable K-maps

		CD			
		00	01	11	10
AB	00	m0	m1	m3	m2
	01	m4	m5	m7	m6
	11	m12	m13	m15	m14
	10	m8	m9	m11	m10

- m0 is $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$.
- m1 is $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D$.
- m2 is $\overline{A} \cdot \overline{B} \cdot C \cdot \overline{D}$.
- m3 is $\overline{A} \cdot \overline{B} \cdot C \cdot D$.

- m4 is $\overline{A} \cdot B \cdot \overline{C} \cdot \overline{D}$.
- m5 is $\overline{A} \cdot B \cdot \overline{C} \cdot D$.
- m6 is $\overline{A} \cdot B \cdot C \cdot \overline{D}$.
- m7 is $\overline{A} \cdot B \cdot C \cdot D$.

- m8 is $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$.
- m9 is $A \cdot \overline{B} \cdot \overline{C} \cdot D$.
- m10 is $A \cdot \overline{B} \cdot C \cdot \overline{D}$.
- m11 is $A \cdot \overline{B} \cdot C \cdot D$.

- m12 is $A \cdot B \cdot \overline{C} \cdot \overline{D}$.
- m13 is $A \cdot B \cdot \overline{C} \cdot D$.
- m14 is $A \cdot B \cdot C \cdot \overline{D}$.
- m15 is $A \cdot B \cdot C \cdot D$.



Don't cares

Sometimes your function has terms that could be 1 or 0 and that doesn't affect your systems output.

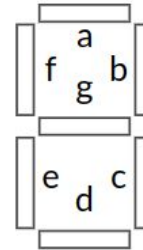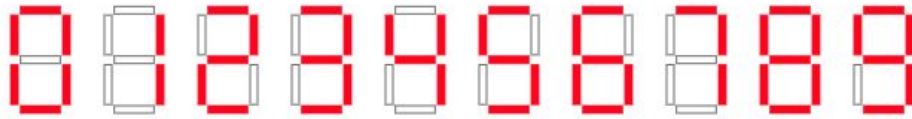Example: Representing digits “0-9”

- Useful for 7-segment displays
- We need 4 inputs (ABCD), segment “a” in the example
- We can represent 0-15 with 4 inputs
- But we don't care from 10 (1010) to 15 (1111)

The digits 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9 can be displayed with seven segments. One possibility is:





Don't cares

Sometimes your function has terms that could be 1 or 0 and that doesn't affect your systems output.

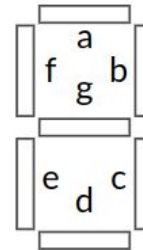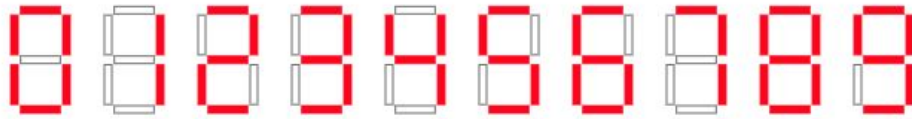Example: Representing digits "0-9"

- Useful for 7-segment displays
- We need 4 inputs (ABCD), segment "a" in the example
- We can represent 0-15 with 4 inputs
- But we don't care from 10 (1010) to 15 (1111)

The digits 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9 can be displayed with seven segments. One possibility is:



		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

Term Summary

- An implicant is a Boolean function term that makes the function true.
 - product/minterm term in Sum of Products (SOP)
 - sum/maxterm term in Product of Sums (POS)
- In an prime implicant, a variable in the expression cannot be removed.
 - A group of square or rectangle made up of bunch of adjacent minterms
 - What is the biggest group can form, 2, 4, 8, 16.
- An essential prime implicant contains a minterm not covered by any other implicant.
 - Always appear in final solution

K-Maps simplification examples

- Extra video lecture
 - $\sim A \sim B \sim C + A \sim B \sim C + A \sim BC$
 - $AB \sim C \sim D + A \sim B \sim C \sim D + ABC \sim D + A \sim BC \sim D$
 - $A \sim B \sim C \sim D + A \sim B \sim CD + A \sim BCD + A \sim BC \sim D + \sim A \sim B \sim C \sim D + \sim A \sim B \sim CD + \sim A \sim BC \sim D + \sim A \sim BCD$



Questions?

- Next: Combinational building blocks
- Multiplex and decoders