



Combinational Logic Building Blocks


Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Combinational Building Blocks

- Combinational logic is often grouped into larger building blocks to build more complex systems.
- This is an application of the principle of abstraction
 - hiding the unnecessary gate-level details to emphasize the function of the building block.
- Two more commonly used building blocks:
 - multiplexers
 - decoders.


Multiplex (MUX)

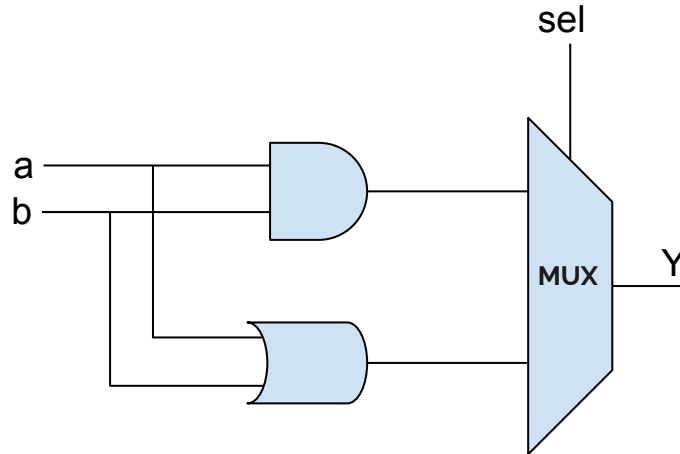- Multiplexers are among the most commonly used combinational circuits.
- They choose an output from among several possible inputs based on the value of a select signal.
- A multiplexer is sometimes affectionately called a mux.



Two to One Multiplexor

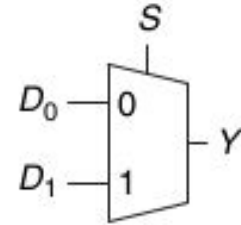
- A two-to-one multiplexor (2-1 or 2:1 MUX) used to combine other blocks
 - inputs D_0 and D_1
 - select input S
 - output Y .
- Similar to an if-then-else.
 - When $S = 0$, $Y = d0$
 - When $S = 1$, $Y = d1$
- The selection circuit can be implemented with a 1-to-2 decoder
- S is also called a control signal




S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Two to One Multiplexor
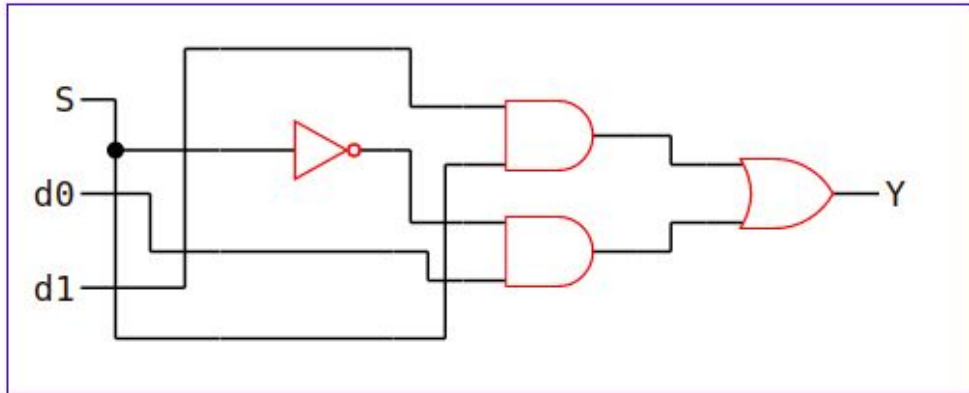
$$Y = \overline{S} \cdot d0 + S \cdot d1$$



		d1, d0			
		00	01	11	10
s	0	0	1	1	0
	1	0	0	1	1

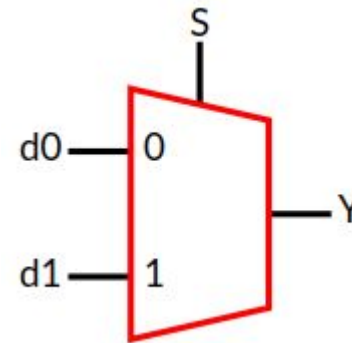

S	d1	d0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Two Variables Boolean Function with 4-1 MUX


- Any two variable Boolean functions can be implemented with a 4-1 MUX. The idea can be extended to more variables.
- The data inputs to the 4-to-1 MUX are set to the truth table entries

Two Variables Boolean Function with 4-1 MUX

- Any two variable Boolean functions can be implemented with a 4-1 MUX. The idea can be extended to more variables.
- The data inputs to the 4-to-1 MUX are set to the truth table entries


AND

a	b	y
0	0	0
0	1	0
1	0	0
1	1	1

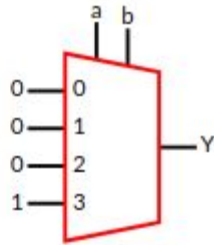

XOR


a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

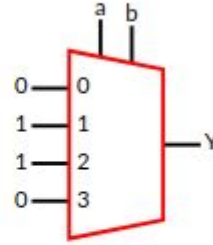

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(a)
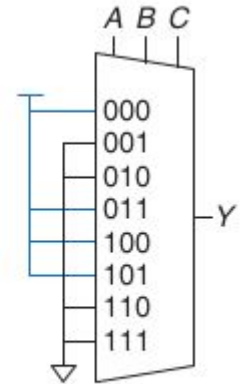
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$




(b)

Decoders

- A decoder has N inputs and 2^N outputs
- Asserts (set it to true) exactly one of its outputs depending on the input combination.
- Used to select only one component in a set
 - e.g. Access multiple memory modules


Decoders

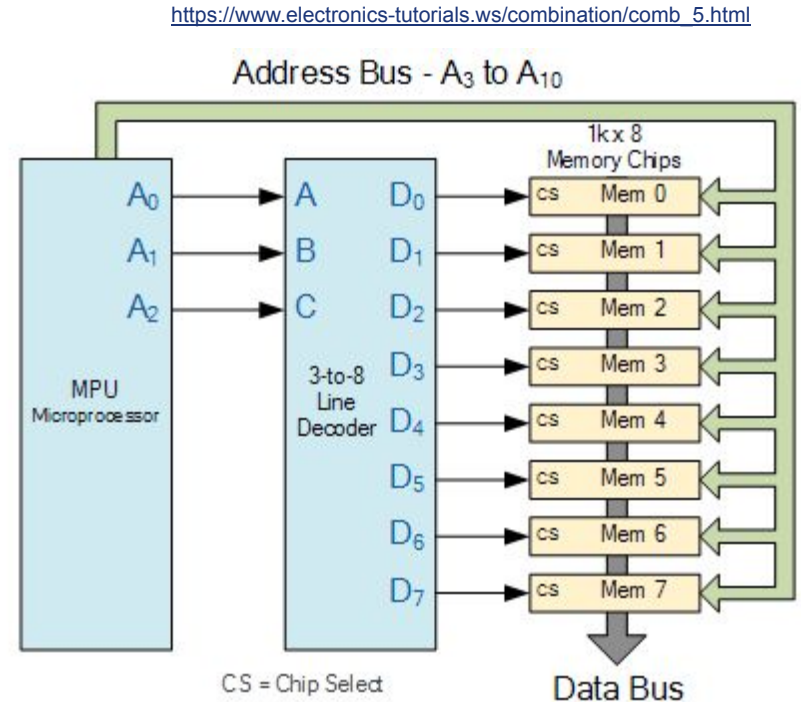- A decoder has N inputs and 2^N outputs
- Asserts (set it to true) exactly one of its outputs depending on the input combination.
- Used to select only one component in a set
 - e.g. Access multiple memory modules



Decoders

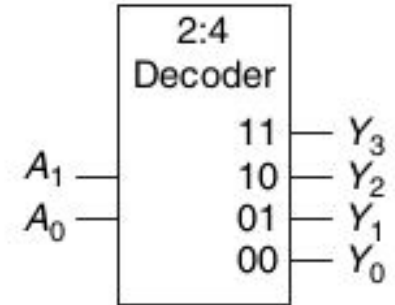- A decoder has N inputs and 2^N outputs
- Asserts (set it to true) exactly one of its outputs depending on the input combination.





A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

One to Two Decoders



- Decoders are used to select one element out of N elements
- A N input decoder can select up to 2^N elements
- Provides all the minterms for the inputs

a	Y0	Y1
0	1	0
1	0	1

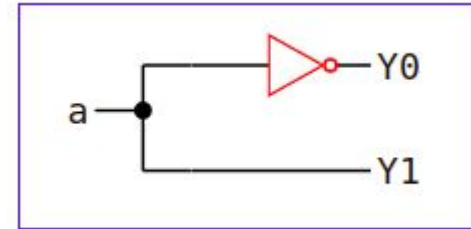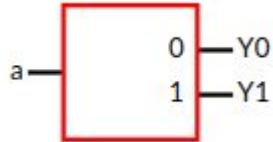

Two to Four Decoders

a	b	Y0	Y1	Y2	Y3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

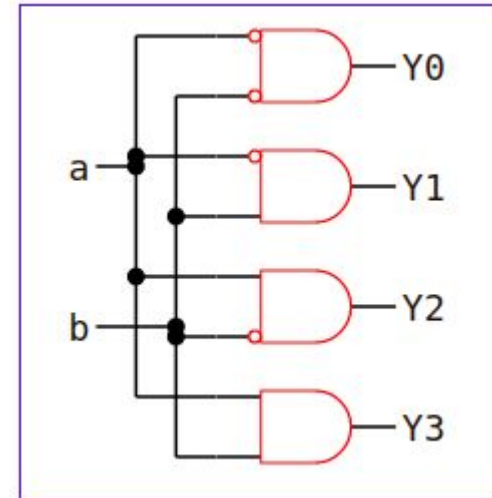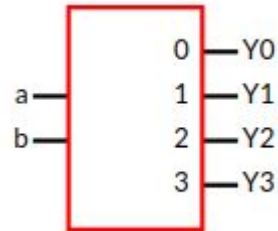

Muxes and Decoders

- Larger and multifunctional designs
- Help group other logic blocs
- Implement functions



Questions?

Next: Bitwise operations