



Design Using Structural and Functional Verilog

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Structural vs Functional Verilog

- Structural
 - customarily, refers to describing a design using module instances
 - lower-level building blocks such as AND gates and flip-flops
- Functional or behavioural
 - refers to describing a design using always comb blocks
 - clock gates and synchronizer cells
- We will compare the many functional representations using the YOSYS tool

Modulus Detector Version 1

- Several ways to describe a combinational logic module
- Consider the following circuit that determines if a 4-bit unsigned integer has a remainder of 1 or 2 after being divided by 3.

$$v \bmod 3 = 1 \text{ or } 2$$

- The four inputs, $v[3]$, $v[2]$, $v[1]$, and $v[0]$ for a unsigned integer

$$8*v[3] + 4*v[2] + 2*v[1] + 1*v[0]$$

- `always_comb`
 - Sensitivity list includes all signals in that function, different from `always @` (next classes)

Modulus Detector Version 1 (case)


mod3_12_v1.v, tb_mod3_12.v

- Truth tables can be represented almost directly with a case statement

```
case ( v )  
    4'b0000: y = 0;  
    4'b0001: y = 1;  
    4'b0010: y = 1;  
    ...  
    4'b1110: y = 1;  
    4'b1111: y = 0;  
endcase
```

v3	v2	v1	v0	y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Modulus Detector Version 1

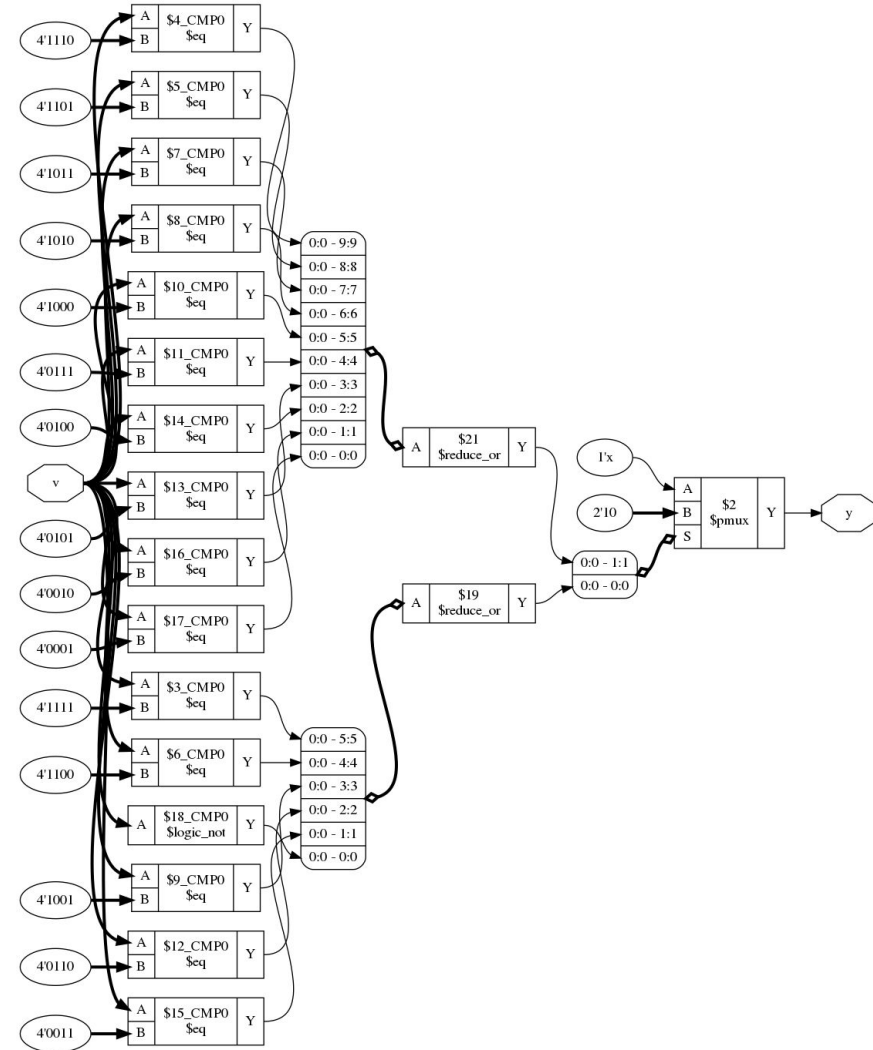


```
casez ( v ) // don't cares


4'b010?: y = 1; // (w3w2-w1) prime implicants
4'b0?01: y = 1;
4'b?101: y = 1;
4'b01?1: y = 1;
4'b?010: y = 1;
4'b1?10: y = 1;
4'b101?: y = 1;
4'b10?0: y = 1;

default: y = 0;

endcase
```

 

Modulus Detector Version 2

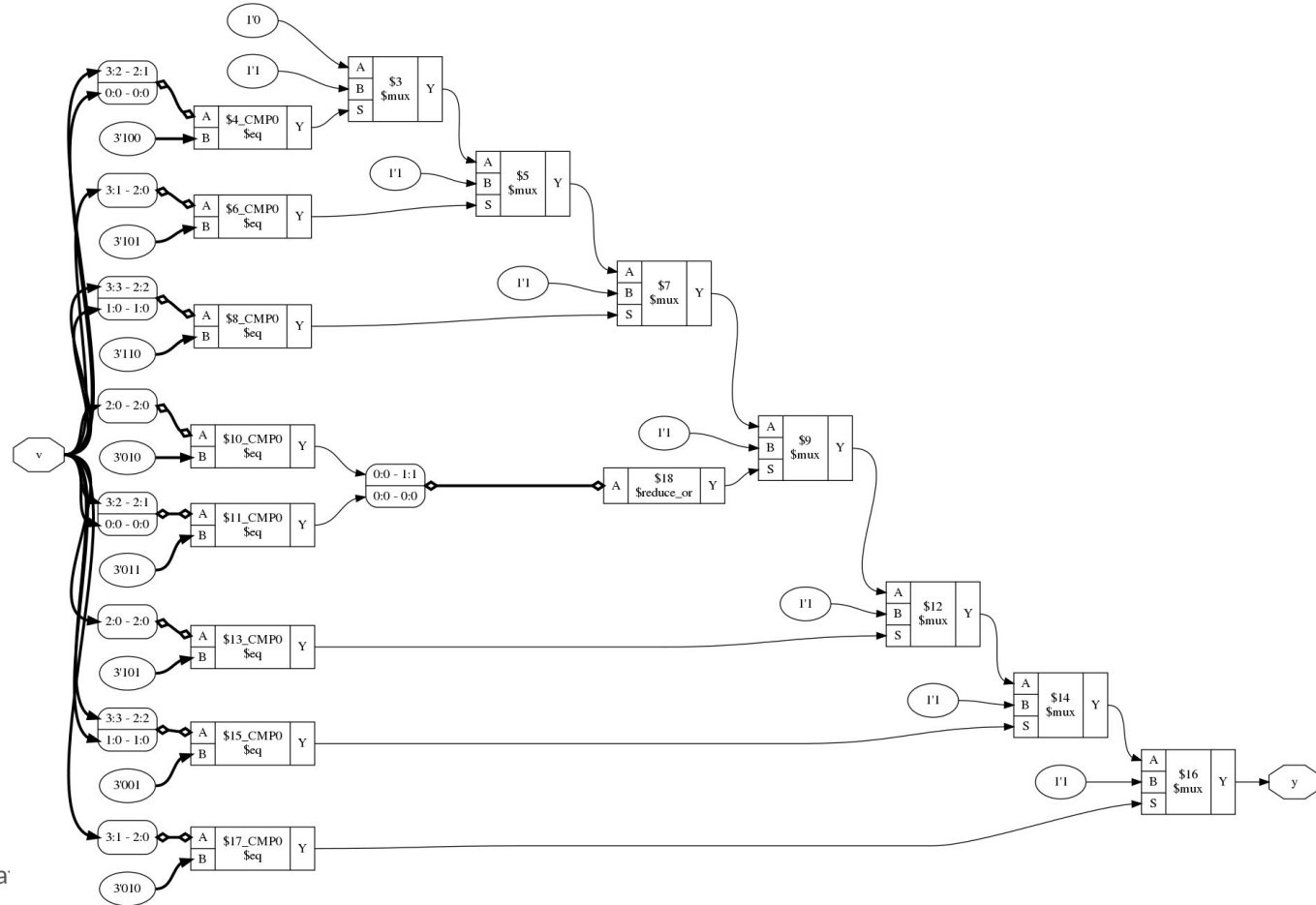


Modulus Detector Version 3 (case, decimals)

- Decimal integers, that represent the 4 bit value, can be used directly

```
case ( v )  
    0,3,6,9,12,15: y = 0;  
    default: y = 1;  
endcase
```

v3	v2	v1	v0	y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Modulus Detector Version 3

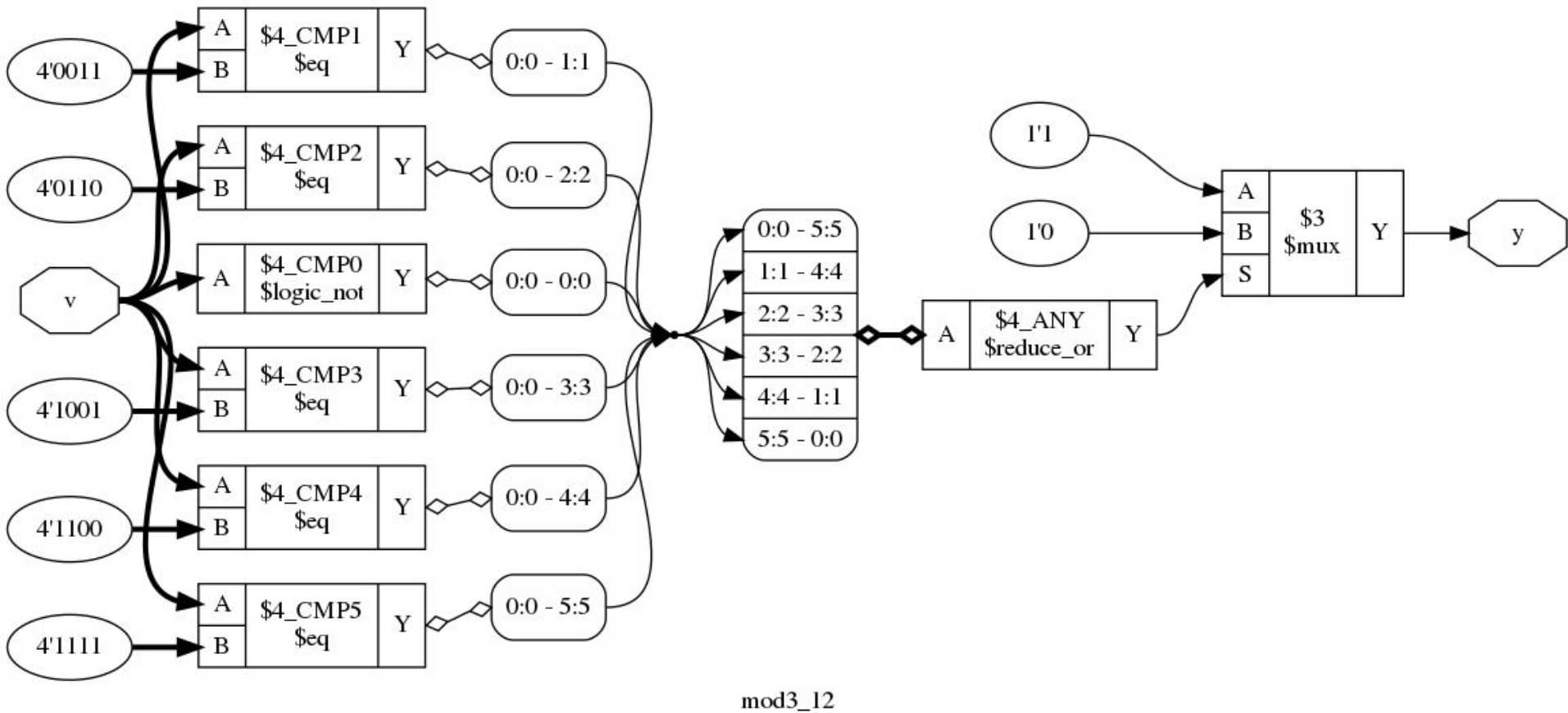


Modulus Detector Version 4 (mod operator)

- Verilog also allows mathematical expressions to be used

```
integer m;  
always_comb begin  
    m = v % 3;  
    y = m == 1 || m == 2;  
end
```

Modulus Detector Version 4

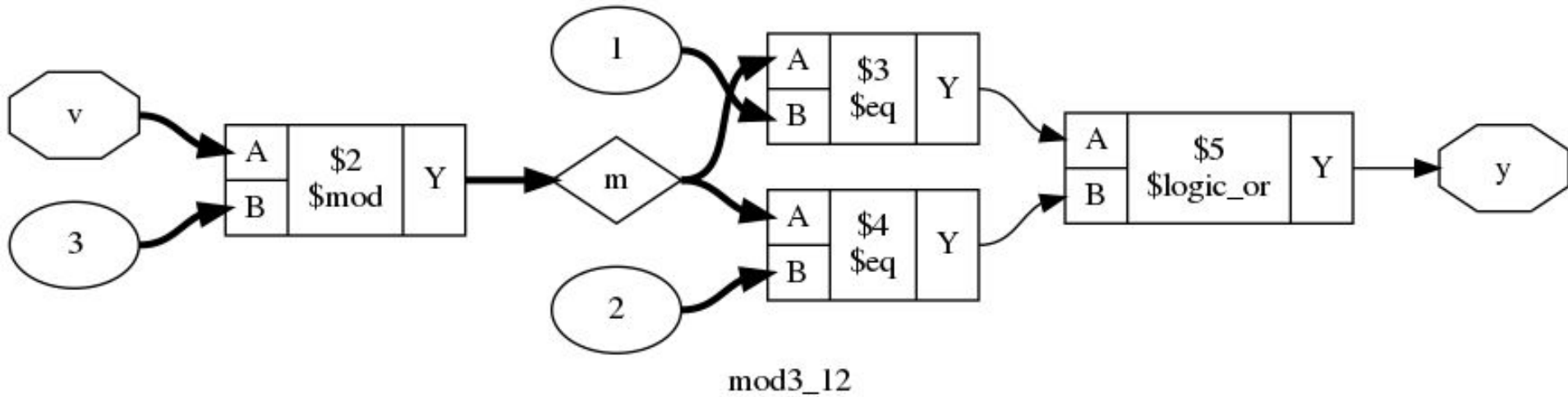


Modulus Detector Version 5 (mod operator 2)

- Really compact version

```
module mod3_12( output logic y, input logic [3:0] v );  
  
    assign y = v % 3 != 0;  
  
endmodule
```

Modulus Detector Version 5

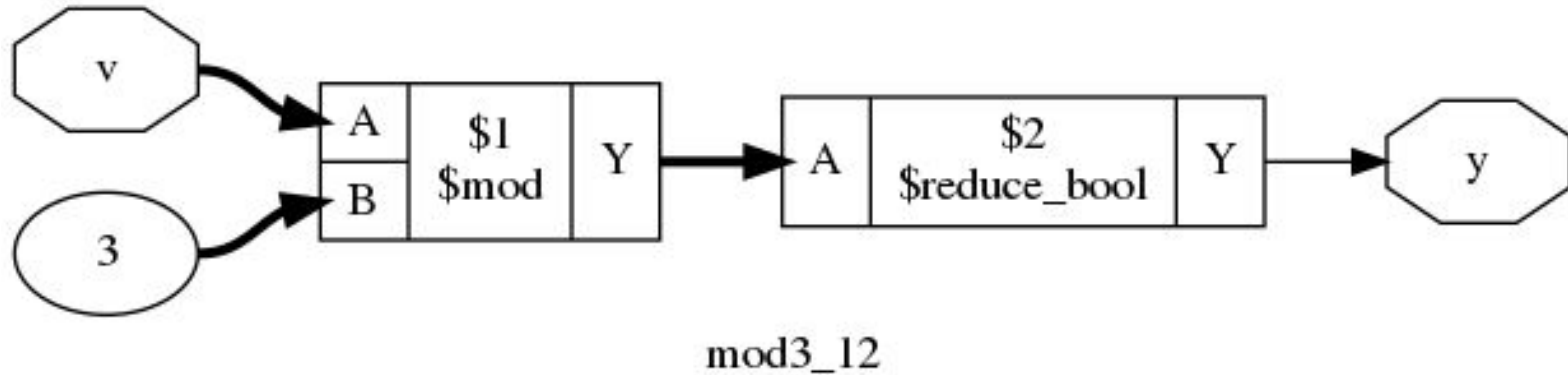


Modulus Detector Version 6 (if else)

- Verilog also provides conditional if statements



```
always_comb begin
    if ( v % 3 == 0 ) begin
        y = 0;
    end
    else begin
        y = 1;
    end
end
```

Modulus Detector Version 6

 


Seven Segment Display (case, all segments)

  - The digits 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9 can be displayed with seven segments
- It also can be implemented using case.



Seven Segment Display

 
```
// {g,f,e,d,c,b,a} == seg
always_comb begin
    case( digit )
        0: seg = 7'b0111111;
        1: seg = 7'b0000110;
        // digits 2,3,4,5,6,7,8,9 are missing
        default: seg = 7'bxxxxxxx;
    endcase
end
```



Parameterized Modules

- Verilog provides parameters to customize a module
- A K-bit 2-to-1 multiplexor can be implemented with:
- out, b and a are buses of K bits
- s selects all bits from a or b at the same time.

 
```
module mux #(parameter K=4) (  
  
    output logic [K-1:0] out,  
  
    input logic [K-1:0] a, b,  
  
    input logic s);  
  
    assign out = s ? b : a;  
  
endmodule
```



Parameterized Modules

- N to 2^N decoder
- N bits selector
- $2N$ bits output, only one bit activated per selector.
 
```
module decoder #(parameter N=2) (  
    output logic [2**N-1 : 0] d,  
    input logic [N-1:0] sel );  
    assign d = 1 << sel;  
endmodule
```





Questions?

Next: 15 - Modeling Synchronous Systems With Verilog