

Adders, Subtractors, Comparators

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Adding One Bit To Another, A Half-Adder

- All the possible additions of two 1-bit numbers expressed in base 2:

$$0 + 0 = 00 (0)$$

$$0 + 1 = 01 (1)$$

$$1 + 0 = 01 (1)$$

$$1 + 1 = 10 (2)$$

- The left most bit in the above binary example is the carry bit.
- The right most bit is the sum bit

Adding One Bit To Another, A Half-Adder

- A table showing the addition of a and b.
- c is the carry out, and s is the sum.
- The carry output is given by

$$a \& b$$


- The sum output is given by

$$a \& b' + a' \& b$$

- equal to

$$a \oplus b$$

SOP	a	b	c	s
$\bar{a} \cdot \bar{b}$	0	0	0	0
$\bar{a} \cdot b$	0	1	0	1
$a \cdot \bar{b}$	1	0	0	1
$a \cdot b$	1	1	1	0

 


Adding One Bit To Another, A Half-Adder

- model half adder using gates

```
module ha_gates( output logic c, s, input logic a, b);  
    and carry(c, a, b);  
    xor sum(s, a, b);  
endmodule
```

SOP	a	b	c	s
$\bar{a} \cdot \bar{b}$	0	0	0	0
$\bar{a} \cdot b$	0	1	0	1
$a \cdot \bar{b}$	1	0	0	1
$a \cdot b$	1	1	1	0

 


Adding One Bit To Another, A Half-Adder

- model half adder using Boolean algebra

```
module ha_boolean( output logic c, s, input logic a, b);  
    assign      c = a & b;  
    assign      s = a ^ b;  
endmodule
```

SOP	a	b	c	s
$\bar{a} \cdot \bar{b}$	0	0	0	0
$\bar{a} \cdot b$	0	1	0	1
$a \cdot \bar{b}$	1	0	0	1
$a \cdot b$	1	1	1	0

 


Adding One Bit To Another, A Half-Adder

- Model half adder using Verilog's "+" operator

```
module ha_functional( output logic c,s, input logic a,b);  
    assign {c, s} = a + b;  
endmodule
```

- The concatenation {c,s} is a 2-bit number

SOP	a	b	c	s
$\overline{a} \cdot \overline{b}$	0	0	0	0
$\overline{a} \cdot b$	0	1	0	1
$a \cdot \overline{b}$	1	0	0	1
$a \cdot b$	1	1	1	0

 

Adding 4-bit Binary Numbers

1 1
0 1 1 0 (6)
+ 0 0 1 1 (3)

1 0 0 1 (9)

Adding 4-bit Binary Numbers

$$\begin{array}{r} 1 \text{ } 1 \\ 0 \text{ } 1 \text{ } 1 \text{ } 0 \text{ } (6) \\ + \text{ } 0 \text{ } 0 \text{ } 1 \text{ } 1 \text{ } (3) \\ \hline 1 \text{ } 0 \text{ } 0 \text{ } 1 \text{ } (9) \end{array}$$

Adding 4-bit Binary Numbers

$$\begin{array}{r} 11 \\ 0110 \text{ (6)} \\ + 0011 \text{ (3)} \\ \hline 1001 \text{ (9)} \end{array}$$

Adding 4-bit Binary Numbers

$$\begin{array}{r} 11 \\ 0110 \text{ (6)} \\ + 0011 \text{ (3)} \\ \hline 1001 \text{ (9)} \end{array}$$

Adding 4-bit Binary Numbers

$$\begin{array}{r} 1\ 1\ 1 \\ 0\ 1\ 1\ 1\ (7) \\ +\ 0\ 0\ 1\ 1\ (3) \\ \hline 1\ 0\ 1\ 0\ (10) \end{array}$$

Adding 4-bit Binary Numbers

$$\begin{array}{r} 1 \text{ } 1 \text{ } 1 \\ 0 \text{ } 1 \text{ } 1 \text{ } 1 \text{ } (7) \\ + 0 \text{ } 0 \text{ } 1 \text{ } 1 \text{ } (3) \\ \hline 1 \text{ } 0 \text{ } 1 \text{ } 0 \text{ } (10) \end{array}$$

Adding 4-bit Binary Numbers

$$\begin{array}{r} 1\ 1\ 1 \\ 0\ 1\ 1\ 1\ (7) \\ +\ 0\ 0\ 1\ 1\ (3) \\ \hline 1\ 0\ 1\ 0\ (10) \end{array}$$

Adding 4-bit Binary Numbers

$$\begin{array}{r} 1\ 1\ 1 \\ 0\ 1\ 1\ 1\ (7) \\ +\ 0\ 0\ 1\ 1\ (3) \\ \hline 1\ 0\ 1\ 0\ (10) \end{array}$$

Full Adder

- Three bits are being added for each of these digits
 - a, b, cin
- For a n-bit number the adder must be able to handle a carry in

SOP	a	b	cin	c	s
$\overline{a} \cdot \overline{b} \cdot \overline{cin}$	0	0	0	0	0
$\overline{a} \cdot \overline{b} \cdot cin$	0	0	1	0	1
$\overline{a} \cdot b \cdot \overline{cin}$	0	1	0	0	1
$\overline{a} \cdot b \cdot cin$	0	1	1	1	0
$a \cdot \overline{b} \cdot \overline{cin}$	1	0	0	0	1
$a \cdot \overline{b} \cdot cin$	1	0	1	1	0
$a \cdot b \cdot \overline{cin}$	1	1	0	1	0
$a \cdot b \cdot cin$	1	1	1	1	1

Full Adder

SOP	a	b	cin	c	s
$\overline{a} \cdot \overline{b} \cdot \overline{cin}$	0	0	0	0	0
$\overline{a} \cdot \overline{b} \cdot cin$	0	0	1	0	1
$\overline{a} \cdot b \cdot \overline{cin}$	0	1	0	0	1
$\overline{a} \cdot b \cdot cin$	0	1	1	1	0
$a \cdot \overline{b} \cdot \overline{cin}$	1	0	0	0	1
$a \cdot \overline{b} \cdot cin$	1	0	1	1	0
$a \cdot b \cdot \overline{cin}$	1	1	0	1	0
$a \cdot b \cdot cin$	1	1	1	1	1

The k-map for the s, sum output is:

three input XOR

$$s = a \oplus b \oplus cin$$

The k-map for the c, carry output is:

$$c = (a \cdot cin) + (b \cdot cin) + (a \cdot b)$$

b, cin

	00	01	11	10
0	0	1	0	1
1	1	0	1	0

b, cin

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

Full Adder

```
module fa_gates( output logic c, s, input logic a, b, cin);
```

```
    ha_gates a1(c1, s0, a, b);
```

```
    ha_gates a2(c2, s, s0, cin);
```

```
    or (c, c1, c2);
```

```
module fa_boolean( output logic c,s, input logic a,b, cin);
```

```
    assign c = a & b | a & cin | b & cin;
```

```
    assign s = a ^ b ^ cin;
```


```
module fa_functional( output logic c,s, input logic a,b,cin);
```

```
    assign {c,s} = a + b + cin;
```

Adding 3-bit Numbers

- A 3-bit adder
 - one half adder
 - two full adders
 - first bit doesn't need cin
- Connected in a chain
- The carry out of the previous adder is connected to the carry in of the next adder.
- More bits, more full-adders
- Parameterized modules

```
module add #(parameter N=4)
```

 

Signed Addition

- All 3-bit two's complement numbers in decimal are:

100 = -4, 101 = -3, 110 = -2, 111 = -1, 000 = 0, 001 = 1, 010 = 2, 011 = 3

- Two's complement binary numbers can be added as if they were unsigned

$$1 + 2 = 001 + 010 = ?$$

$$-2 + 1 = 110 + 001 = ?$$

$$-1 + 1 = 111 + 001 = ?$$

$$6 - 2 = 0110 - 1110 = ?$$

Signed Addition

- All 3-bit two's complement numbers in decimal are:

100 = -4, 101 = -3, 110 = -2, 111 = -1, 000 = 0, 001 = 1, 010 = 2, 011 = 3

- Two's complement binary numbers can be added as if they were unsigned

$$1 + 2 = 001 + 010 = 011 = 3_{10}$$

$$-2 + 1 = 110 + 001 = 111 = -1_{10}$$

$$-1 + 1 = 111 + 001 = 1000 = 0 \text{ // correct, the 4th bit is ignored (carry)}$$

$$6 - 2 = 0110 + 1110 = 10100 = 4 \text{ // correct, the 5th bit is ignored (carry)}$$

Signed Addition

- It is possible to add two number where the result will overflow
 - $(MSBa == MSBb) \ \&\& \ (MSBout != MSBa)$
- Overflows when addition two positives yield a negative:
 $2 + 2 = 010 + 010 = 100 = 4_{10} (?)$
 $(0 == 0) \ \&\& \ (1 != 0) // \text{Overflow}$
- Overflows when addition two negatives yield a positive:
 $-3 + -2 = 101 + 110 = 1\ 011 = 3_{10} // \text{the 4th bit is ignored}$
 $(1 == 1) \ \&\& \ (0 != 1) // \text{Overflow}$
- Will require a circuit to detect these situations



Building A Subtractor

- Complementing the subtrahend and then doing the addition.
- Use an adder with a two's complement circuit
- A two's complement can be performed by
 - one's complement
 - followed by addition by 1
- A one's complement is done by inverting all the bits with NOT gates.

```
// least significant bit with 1 on carry in
not (invert_b[0], b[0]);
fa bits0 ( carries[0], diff[0], a[0], invert_b[0], 1'b1 );
```

Building An Adder/Subtractor

  - Using a **flag (subtract)** to indicate when we want to do each operation
- XOR will invert the b operand if flag “subtract” is 1



```
xor neg ( invert_b[i], b[i], subtract);
```

```
fa bits ( carries[i+1], result[i], a[i], invert_b[i], carries[i] );
```


- If subtract is 1, b will be two-complement, subtraction

```
fa bits0 ( carries[0], diff[0], a[0], invert_b[0], subtract);
```

- Otherwise it proceed with a regular addition

Zero Detector

 - Another common logic/arithmetic operation
- Usually outputs is high if the input is all zeros
- Given an 8-bit binary number, a zero can be detected with:



- Verilog example in the notes

Equality Checking

- Checking to see if two numbers are the same is another common operation
- This check can be done with a set of XOR gates, one for each bit, and a zero detector

$$0 \text{ xor } 0 = 0$$

$$1 \text{ xor } 1 = 0$$

- Detect zeros for all bits = both operands are the same
- Verilog example in the notes

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

Less/Greater Than Comparison

- Compare number for less than, greater than, or equal
- Hardware that subtracts two binary numbers can be used to test which number is smaller/larger
 - If the result of $A-B$ is negative then A is smaller B .
 - If $A-B$ is positive, then A is larger than B .
 - If $A-B$ is zero, then A is equal to B
- Verilog example in the notes

Next Steps

- Run the examples in the online notes
- Memory in verilog
- Design of a mini datapath