



Combinational Logic

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Combinational Logic Circuit



A **digital logic circuit** is a **combinational logic circuit** if the values of the outputs depend only on the current values of the inputs. Combinational circuits have no memory.

Combinational and Sequential Circuits

- Combinational circuits
 - Output depends only on the current input values.
 - Memoryless.
- Sequential circuits
 - Output depends both on the current and past.
 - Has some memory.
- Important to differentiate

Combinational Logic Circuit

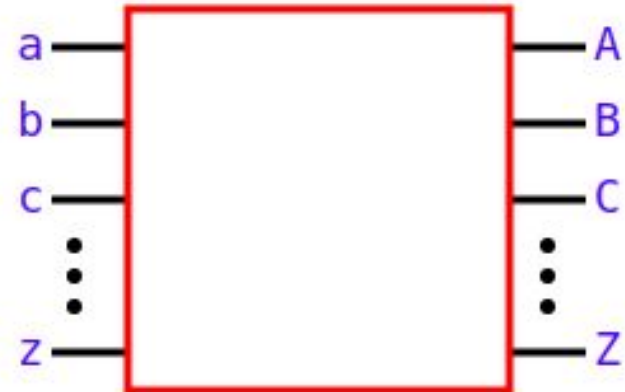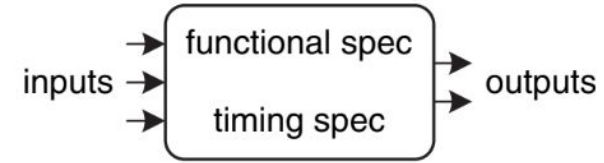- One or more input terminals (ports)
- One or more output terminals
- A functional description
 - In terms of current input.
 - Described by a truth table.
 - Boolean equation.
- A timing description (maximum delay)
 - Lower and upper bounds expected.
 - From input to the output.
- Abstraction
- Black-box idea



Combinational Logic Circuit

- One or more input terminals (ports)
- One or more output terminals
- A functional description
 - In terms of current input.
 - Described by a truth table.
 - Boolean equation.
- A timing description (maximum delay)
 - Lower and upper bounds expected.
 - From input to the output.
- Abstraction
- Black-box idea



$$Y = F(A, B) = A + B$$



(a)




(b)




$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Combinational Logic Circuit

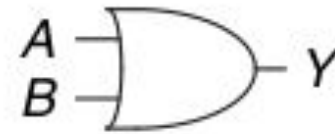- One or more input terminals (ports)
- One or more output terminals
- A functional description
 - In terms of current input.
 - Described by a truth table.
 - Boolean equation.
- A timing description (maximum delay)
 - Lower and upper bounds expected.
 - From input to the output.
- Abstraction
- Black-box idea





(a)

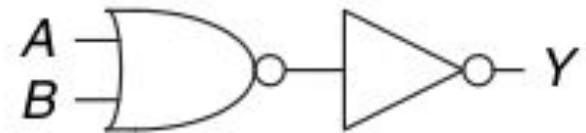

(b)


Combinational Logic Circuit

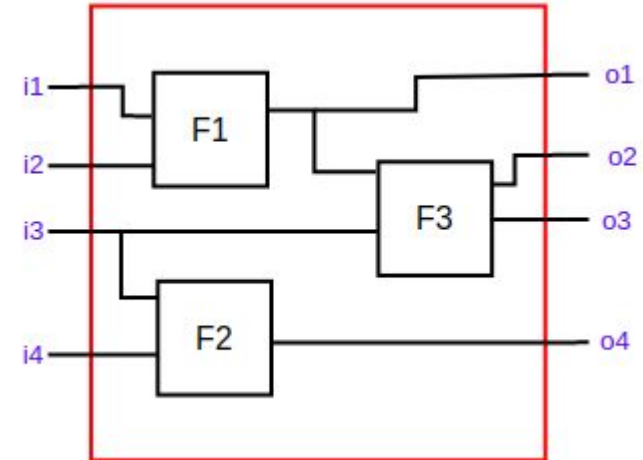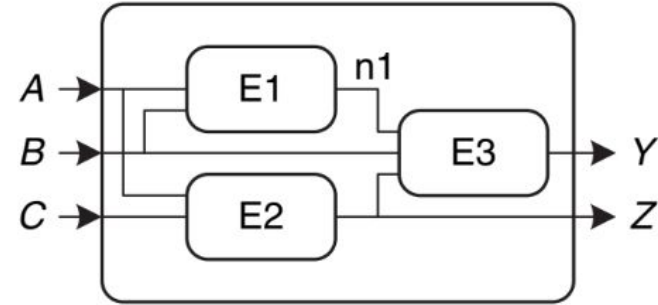- Composed of smaller combinational circuits (sub-circuits)
- The larger circuit is combinational if the sub-circuits are combinational.
- Every sub-circuit must be combinational.
- A wire in the circuit (node)
 - Is controlled by the input;
 - or by the output other sub-circuits.
- No cyclic paths in the circuit (feedback)



Combinational Logic Circuit

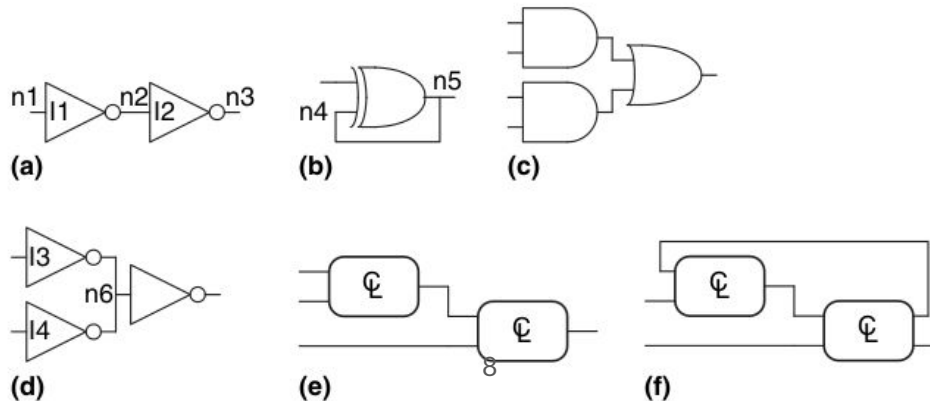- Composed of smaller combinational circuits (sub-circuits)
- The larger circuit is combinational if the sub-circuits are combinational.
- Every sub-circuit must be combinational.
- A wire in the circuit (node)
 - Is controlled by the input;
 - or by the output other sub-circuits.
- No cyclic paths in the circuit (feedback)



Example Combinational Circuits and Boolean Functions


- Variables (a, b, c, cin, ...) are the inputs
- Operators (“·”, “+”, “not”, ...) are the gates
- Function (Y, g7, cout, ...) is the output
- The circuit is drawn by first using NOT gates to invert any input is complemented (i.e., have an over line). Then the operators are changed to their matching gate.

$$g7 = \overline{(\bar{a} \cdot b) \oplus (\bar{b} \cdot a)}$$

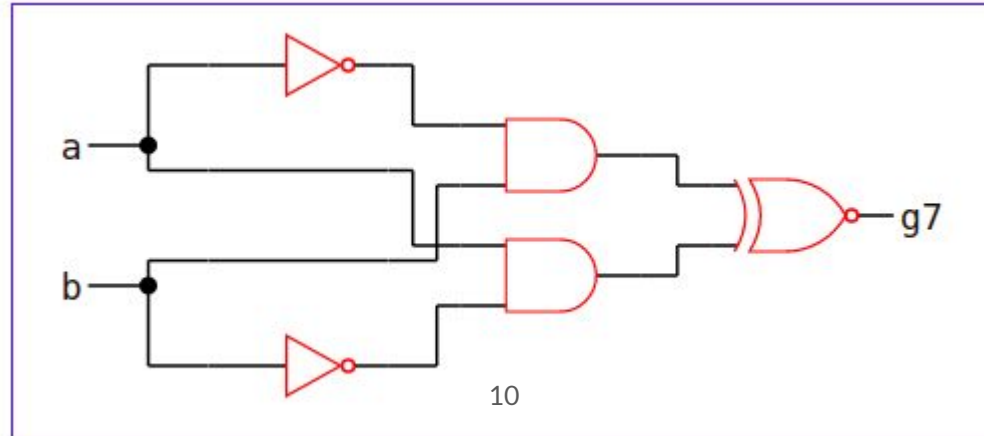
Example Combinational Circuits and Boolean Functions

- Variables (a, b, c, cin, ...) are the inputs
- Operators (“·”, “+”, “not”, ...) are the gates
- Function (Y, g7, cout, ...) is the output
- The circuit is drawn by first using NOT gates to invert any input is complemented (i.e., have an over line). Then the operators are changed to their matching gate.

$$g7 = \overline{(\bar{a} \cdot b)} \oplus (\bar{b} \cdot a)$$



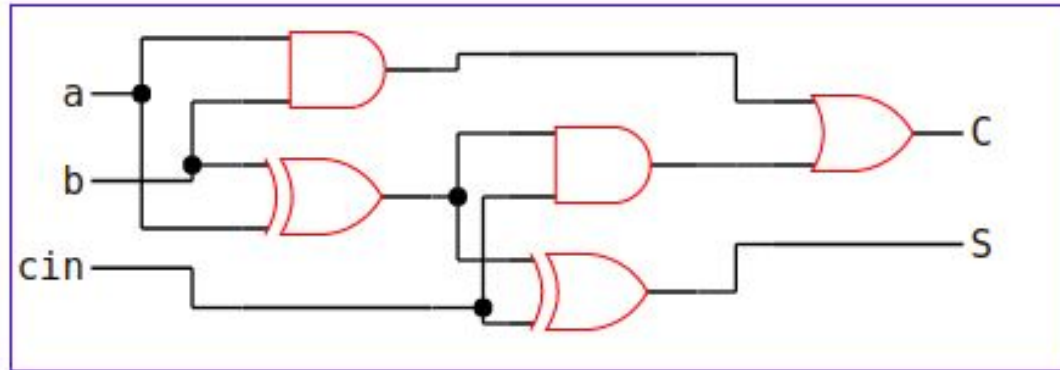
Example Combinational Circuits and Boolean Functions



Example Combinational Circuits and Boolean Functions

$$C = (a \cdot b) + ((a \oplus b) \cdot cin)$$

$$S = ((a \oplus b) \oplus cin)$$

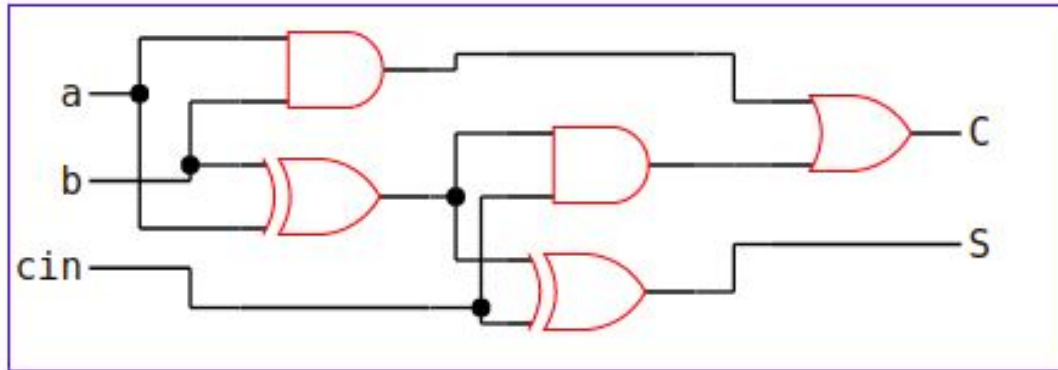



Questions?

- Next: Boolean algebra
- Rules and identities
- Simplification