



# Digital Design with Truth tables and K-Maps

Instructor: Dr. Vinicius Prado da Fonseca ([vpradodafons@online.mun.ca](mailto:vpradodafons@online.mun.ca))

# Digital Design

---

Translate the problem's definition into a circuit using gates

Set of steps that translates a problem into gates:

- Use a truth table to describe a solution to the problem.
- Write the truth table as a K-map.
- Use the K-map to produce a minimized Boolean expression.
- Use the Boolean expression to design a circuit.
- Run the examples using the course repo/devcontainer

# Circuit to detect $2 \leq (a, b, c) \leq 5$

- Detects the range 2 to 5
- Each row of the table can represent an integer,  $000_2 = 0_{10}, 001_2 = 1_{10}, \dots, 111_2 = 7_{10}$

# Circuit to detect $2 \leq (a, b, c) \leq 5$

- Detects the range 2 to 5
- Each row of the table can represent an integer, 000 = 0, 001 = 1, ... 111 = 7



a	b	c	e
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

# Circuit to detect $2 \leq (a, b, c) \leq 5$

	bc			
	00	01	11	10
a				
0	0	0	1	1
1	1	1	0	0

	bc			
	00	01	11	10
a				
0	0	0	1	1
1	1	1	0	0
  
$$\bar{a} \cdot b + a \cdot \bar{b} = a \oplus b.$$




- Verilog implementation

a	b	c	e
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
 
# Circuit to detect $2 \leq (a, b, c) \leq 5$ (Verilog)


```
module detect2_5(output logic y, input logic a, b, c);  
    logic o1, o2, nota, notb;  
    not #2 n1(nota, a);  
    not #2 n2(notb, b);  
    and #2 a1(o1, nota, b);  
    and #2 a2(o2, notb, a);  
    or #2 or1(y, o1, o2);  
endmodule
```

$$\bar{a} \cdot b + a \cdot \bar{b} = a \oplus b.$$



```
module detect2_5(output logic y, input logic a, b, c);  
  
    xor #2 x1(y, a, b);  
  
endmodule
```
 
```
module detect2_5(output logic y, input logic a, b, c);  
  
    assign y = a ^ b;  
  
endmodule
```



# Circuit to detect $2 \leq (a, b, c) \leq 5$ (Verilog tb)

```
`timescale 1ns / 1ns

module main;
    logic a, b, c, f;
    integer all_inputs, i;

    detect2_5 dut (f, a, b, c);

    assign {a,b,c} = all_inputs[2:0];

    initial begin
        $display("t=%04d abc f", $time);
        i = 0;
        repeat ( 8 ) begin
            all_inputs = i;

            #10;
            $display("t=%04d %b%b%b %b", $time, a, b, c, f);
            i = i + 1;
        end
    end
endmodule
```

# Add 3 to 3-bits

---

The truth table for a 3-input 3-output circuit that adds 011 ( $3_{10}$ )

We have 3 outputs, 3 equations: x, y and z.



# Add 3 to 3-bits

The truth table for a 3-input 3-output circuit that adds 011 ( $3_{10}$ )

We have 3 outputs, 3 equations: x, y and z.

a	b	c	x	y	z
0	0	0	0	1	1
0	0	1	1	0	0
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	0	0	1
1	1	1	0	1	0

# Add 3 to 3-bits

The truth table for a 3-input 3-output circuit that adds 011 ( $3_{10}$ )

x=

		bc			
		00	01	11	10
a	0	m0	m1	m3	m2
	1	m4	m5	m7	m6

y=

		bc			
		00	01	11	10
a	0	m0	m1	m3	m2
	1	m4	m5	m7	m6

z=

		bc			
		00	01	11	10
a	0	1	0	0	1
	1	1	0	0	1

a	b	c	x	y	z
0	0	0	0	1	1
0	0	1	1	0	0
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	0	0	1
1	1	1	0	1	0


# Add 3 to 3-bits

The minimized Boolean expressions are:

$$x = a \cdot \bar{b} \cdot \bar{c} + \bar{a} \cdot c + \bar{a} \cdot b$$


$$y = \bar{b} \cdot \bar{c} + b \cdot c$$

$$z = \bar{c}$$

 

# Add 3 to 3-bits

```
module add_3(output logic x, y, z, input logic a, b, c);  
  
    logic n_a, n_b, n_c;  
    logic i_0, i_1, i_2, i_3, i_4;  
  
    not (n_a, a);  
    not (n_b, b);  
    not (n_c, c);  
  
    and a_0(i_0, a, n_b, n_c);  
    and a_1(i_1, n_a, c);  
    and a_2(i_2, n_a, b);  
    and a_3(i_3, n_b, n_c);  
    and a_4(i_4, b, c);  
  
    or (x, i_0, i_1, i_2); // x = a&~b&~c | ~a&c | ~a&b  
    or (y, i_3, i_4);     // y = ~b&~c | b&c  
  
    buf (z, n_c);         // z = ~c  
endmodule
```

 

# Add 3 to 3-bits

Functional verilog using Boolean expressions:

```
module add_3(output logic x, y, z, input
logic a, b, c);
    assign x = a&~b&~c | ~a&c | ~a&b;
    assign y = ~b&~c | b&c;
    assign z = ~c;
endmodule
```

$$\begin{aligned}x &= a \cdot \overline{b} \cdot \overline{c} + \overline{a} \cdot c + \overline{a} \cdot b \\y &= \overline{b} \cdot \overline{c} + b \cdot c \\z &= \overline{c}\end{aligned}$$

# Add 3 to 3-bits

## Testbench

```
`timescale 1ns/1ns

module main;
    logic a, b, c;
    logic x, y, z;
    integer all_inputs, i;


    add_3 dut(x,y,z,a,b,c);

    assign {a,b,c} = all_inputs[2:0];

    initial begin
        i = 0;
        #10 $display("t=%04d abc xyz", $time);
        repeat (8) begin
            all_inputs = i;
            #10 $display("t=%04d %b%b%b %b%b%b", $time, a, b, c, x, y, z);
            i = i + 1;
        end
    end
endmodule
```

 
# Seven Segment Displays (segment a) [HERE]

The digits 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9 can be displayed with seven segments


 
# Seven Segment Displays (segment a)

- The seven segments can be labeled with a, b, c, d, e and f
- The digit 1 is displayed when segments b and c are turned on





# Seven Segment Displays (segment a)

The K-map for the a-segment controller is:

CD

	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	0	0	0
10	1	1	0	0

AB

A	B	C	D	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1

# Seven Segment Displays (segment a)

The prime implicants are:


$$\overline{A} \cdot \overline{B} \cdot \overline{D}, \overline{B} \cdot \overline{C} \cdot \overline{D}, A \cdot \overline{B} \cdot \overline{C}, \overline{A} \cdot C, \text{ and } \overline{A} \cdot B \cdot D$$

The essential prime implicants:

$$A \cdot \overline{B} \cdot \overline{C}, \overline{A} \cdot C, \text{ and } \overline{A} \cdot B \cdot D$$

One possible minimal Boolean expression is:

 
$$A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot C + \overline{A} \cdot B \cdot D + \overline{A} \cdot \overline{B} \cdot \overline{D}$$


 
# Seven Segment Displays (segment a)

```
module seg_a(output logic out_a, input logic a, b,  
c, d);  
  
    logic n_a, n_b, n_d;  
    logic i_0, i_1, i_2, i_3;  
  
    not (n_a, a);  
    not (n_b, b);  
    not (n_c, c);  
    not (n_d, d);  
  
    and a_0(i_0, a, n_b, n_c);  
    and a_1(i_1, n_a, c);  
    and a_2(i_2, n_a, b, d);  
    and a_3(i_3, n_d, n_b, n_a);  
  
    or (out_a, i_0, i_1, i_2, i_3);  
  
endmodule
```

$$A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot C + \overline{A} \cdot B \cdot D + \overline{A} \cdot \overline{B} \cdot \overline{D}$$




# Don't Cares in Truth Tables

- 4-bit -> 16 possible values.
- 3-bit -> 8 possible values
- Ten decimal digits only require 10 values.
- 6 values -> don't care values
  - 11 - 15
  - Can be used to further simplify the Boolean expression
- A K-map with don't cares for the a-segment is:

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X
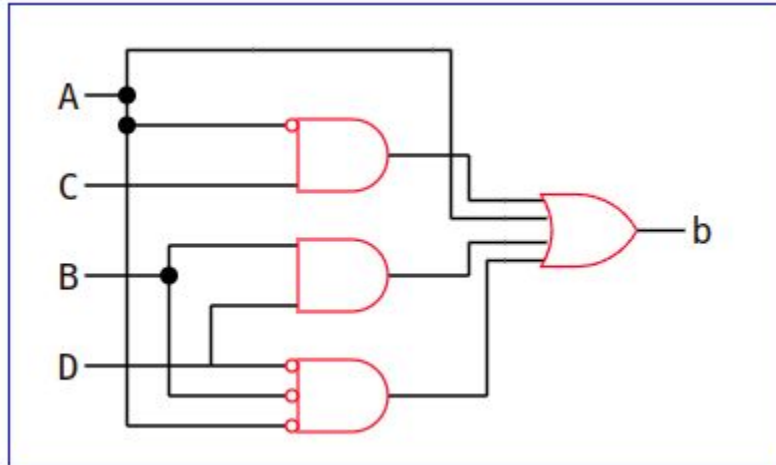
# Don't Cares in Truth Tables

$$A + B \cdot D + \bar{A} \cdot C + \bar{A} \cdot \bar{B} \cdot \bar{D}$$



		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

# Don't Cares in Truth Tables

```
module seg_a(output logic out_a, input logic a, b, c, d);  
  
    assign out_a = c | a | b&d | ~b&~d; // not same as notes  
    //assign out_a = a | b&d | ~a&c | ~a&~b&~d;  
  
endmodule
```

Truth Table for  $out_a = c | a | b \& d | \sim b \& \sim d$ :



	CD			
	00	01	11	10
AB	00	1	0	1
	01	0	1	1
	11	0	0	0
	10	1	1	0

Truth Table for  $out_a = a | b \& d | \sim a \& c | \sim a \& \sim b \& \sim d$ :

	CD			
	00	01	11	10
AB	00	1	0	1
	01	0	1	1
	11	X	X	X
	10	1	1	X

# Don't Cares in Truth Tables

Before and after

  

# Online notes

---

- More examples
  - Practice implementing in verilog
  - Previous lecture, 10 - Verilog For Combinational Logic, also has some examples
  - Use the repo and devcontainer
- Last Unit 2 lecture





# Questions?

Next: Unit 3, Sequential Logic, FSM

# Lab 3 material

---

- Here we finish the lab 3 material
- Get the lab manual from:

Contents > Labs > Lab support files > Lab Manual