



Micro Architecture Of ARM

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Microarchitecture

- Microarchitecture is the connection between logic and architecture.
- Specific arrangement.
 - Registers
 - ALUs
 - Finite state machines (FSMs)
 - Memories
 - other logic building blocks (e.g. Multiplexers)

Microarchitecture

- A particular architecture, such as ARM, may have many different microarchitectures, each with different trade-offs of performance, cost, and complexity.
- They all run the same programs, (based on the same ISA) but their internal designs vary widely.

Microarchitecture

- Design an ARM CPU that implements:
 - Data processing instructions:
 - ADD
 - SUB
 - AND
 - ORR
 - Memory instructions:
 - LDR
 - STR
 - Unconditional branch:
 - B

Review of Fetch/Execute

The CPU controls the operations of a computer by fetching instructions indexed by the Program Counter (PC) from memory.

An instruction can cause the CPU to:

- Load data from memory
- Store data to memory
- Perform data operations on the register file (working storage)
- Conditional change the PC

Review of Fetch/Execute

- The fetch/execute algorithm that depicts the operations of a CPU
- The following single cycle CPU implements both the fetch and execute in one cycle
- One cycle execution requires two separate memories, one to provide the instruction and one for data
- All info I need is in the instruction itself
 - Controller splits the instruction

```
while the computer has power:
```


```
    IR <= Memory[PC]
```

```
    Decode and execute the  
    instruction in the IR
```

```
    Adjust the PC
```


```
end while
```

Control Lines

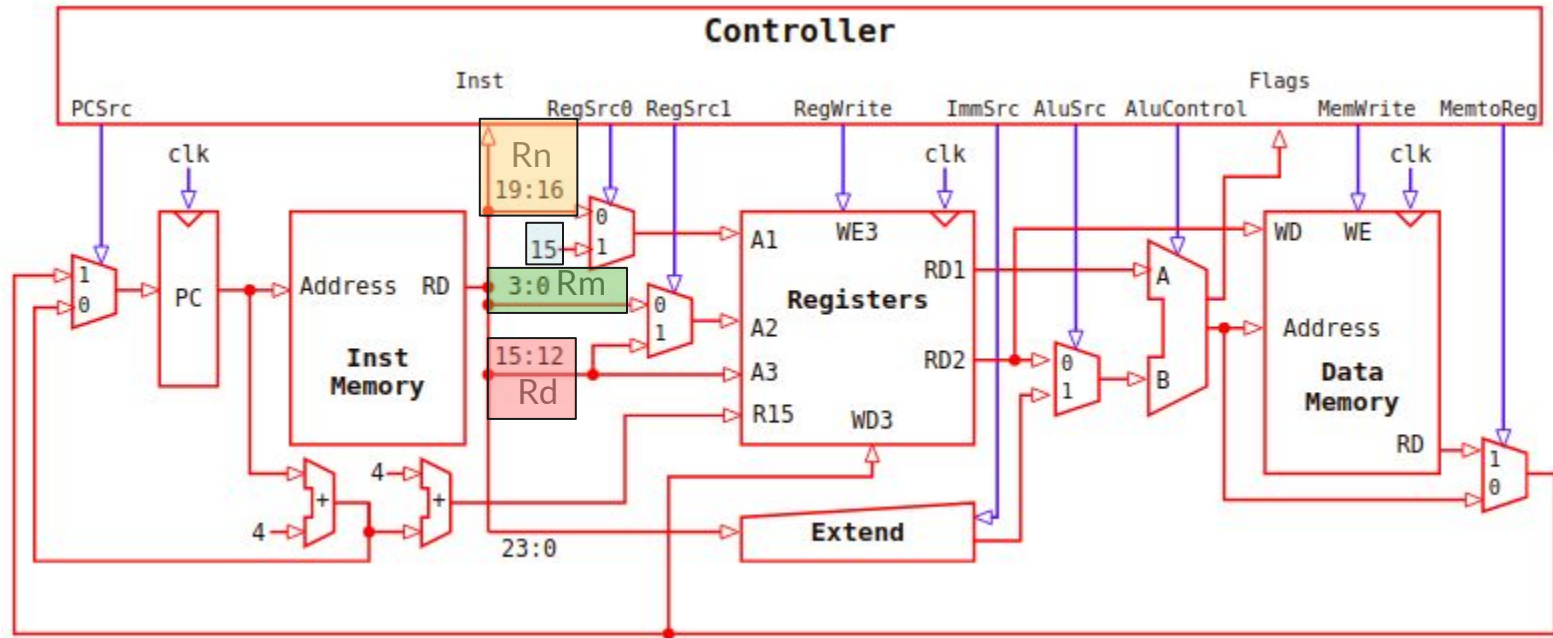

Control Lines - PCSrc

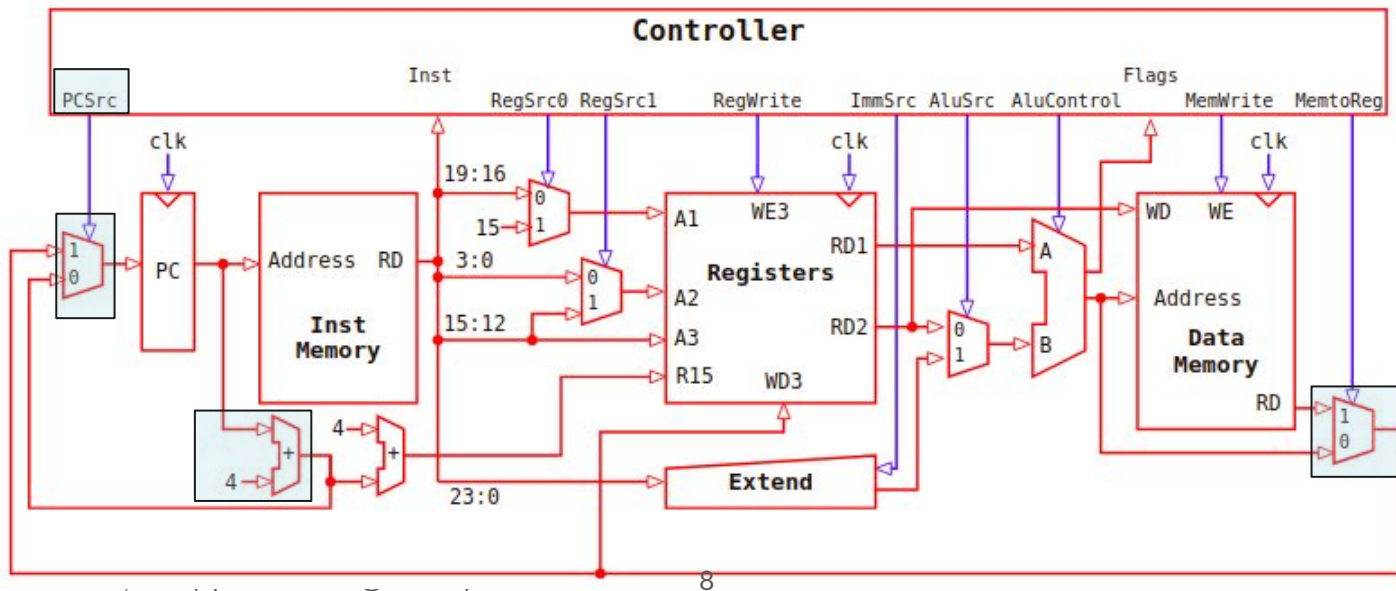- Controls a multiplexor that selects the PC+4 when 0
- otherwise the output of the ALU is selected.
- Branch Example on slide 32



31:28		25		24:21		20		19:16		15:12		11:0			
cond		00		I		cmd		S		Rn		Rd		Src2	

I=1 rot=11:8 immed8=7:0


rot	immed8
-----	--------

I=0 sham5=11:7 sh=6:5 Rm=3:0

sham5	sh	0	Rm
-------	----	---	----

Control Lines - RegSrc0

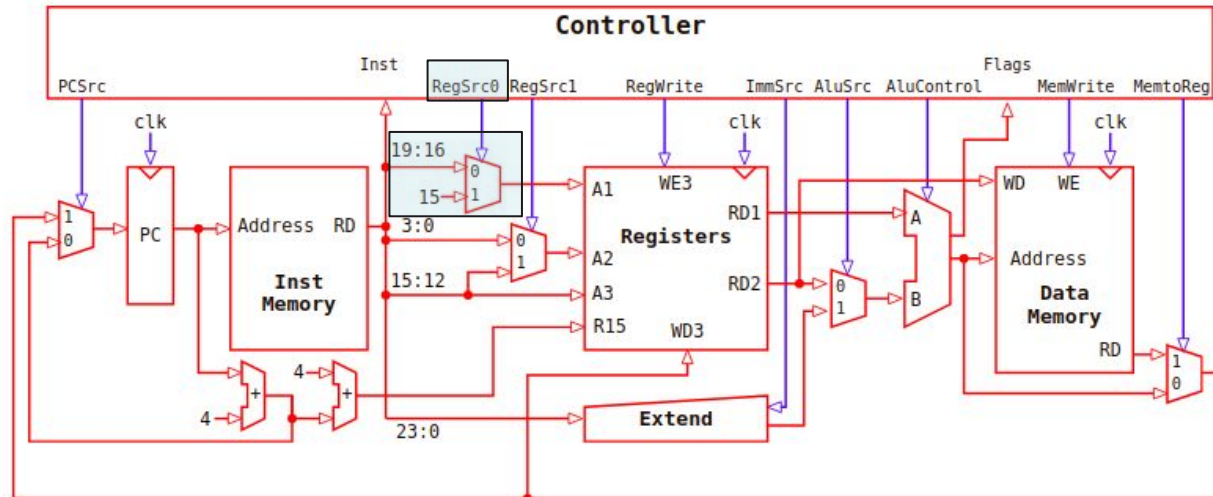- Controls whether the PC (R15) is selected when 1
 - otherwise bits [19:16] are selected
- These bits select the Rn, the first operand of the ARM instructions or R15
- R15 is selected for the branch instruction



31:28	25	24:21	20	19:16	15:12	11:0
cond	00	I	cmd	S	Rn	Rd
						Src2

Control Lines - RegSrc1


I=1 rot=11:8 immed8=7:0

rot	immed8
-----	--------

I=0 shamt5=11:7 sh=6:5 Rm=3:0

shamt5	sh	0	Rm
--------	----	---	----

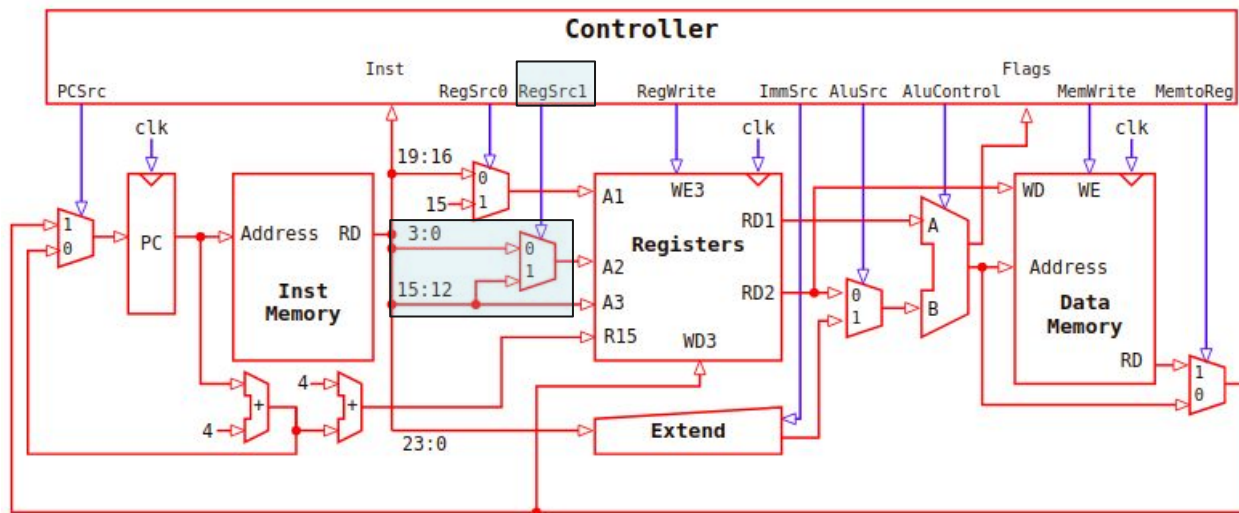- Controls whether the Rd or Rm register is selected.
- The control is 0 when Rm is selected, otherwise Rd is selected (str instruction, format later).



31:28	25	24:21	20	19:16	15:12	11:0
cond	00	I	cmd	S	Rn	Rd
						Src2

I=1 rot=11:8 imm8=7:0


rot	imm8
-----	------

I=0 shamt5=11:7 sh=6:5 Rm=3:0

shamt5	sh	0	Rm
--------	----	---	----


Control Lines - RegSrc1

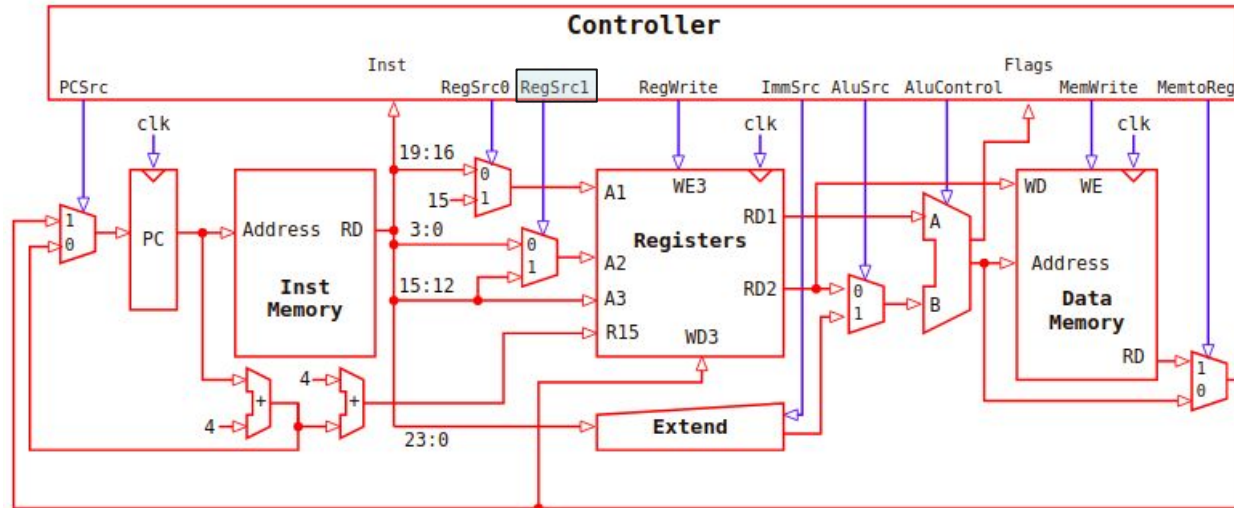- The data processing instructions set control to 0.
- The store memory instructions sets the control to 1.
- Any instruction that uses immediate data is a do not care.




Control Lines - RegWrite

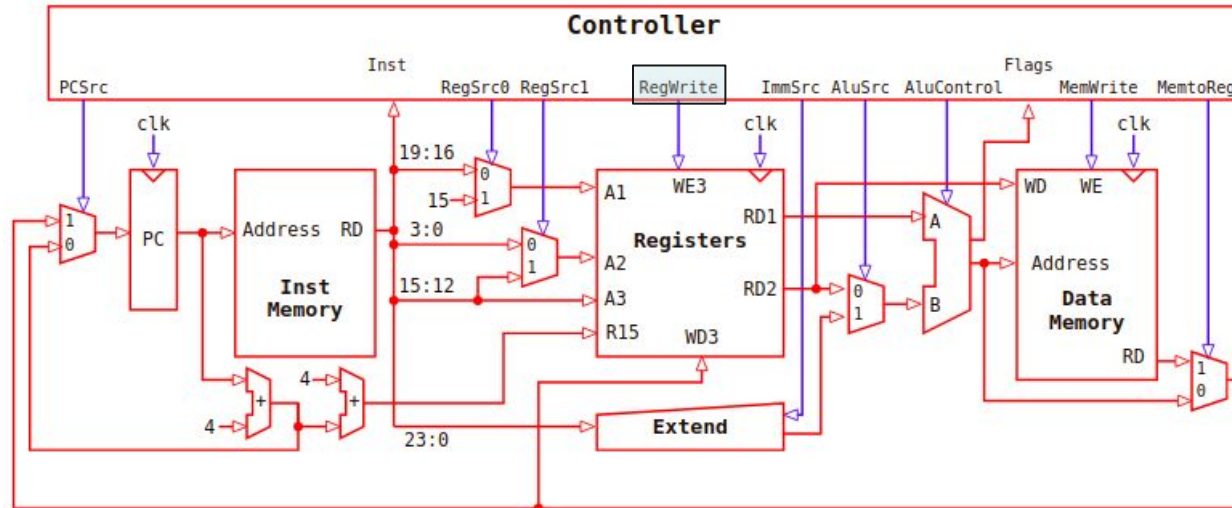- The register file is updated with RegWrite is set to 1
 - otherwise no register is updated




Control Lines - ImmSrc

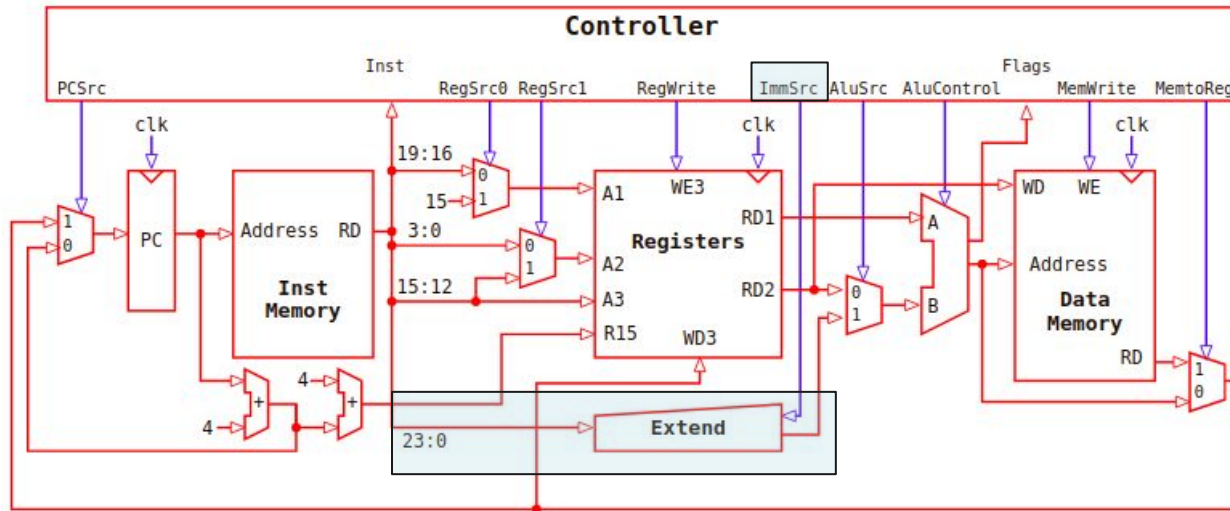- Selects between zero extending bits [7:0] for the data processing instructions
- Zero extending bits [11:0] for the memory instructions
- Sign extending bits [23:0] and multiply by 4 for the branch instructions
- The controls are DATA, MEM and B




Control Lines - AluSrc

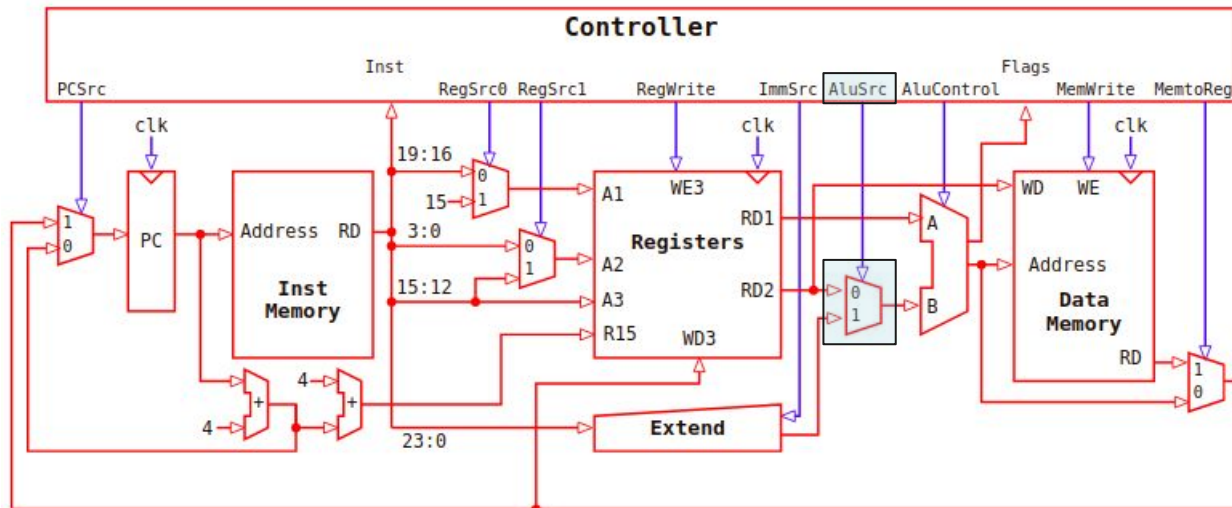- Selects between read data port 2 (RD2)
 - or the result of the extend module
- The register is selected with the control is 0
 - otherwise the immediate extend module is selected




Control Lines - AluSrc

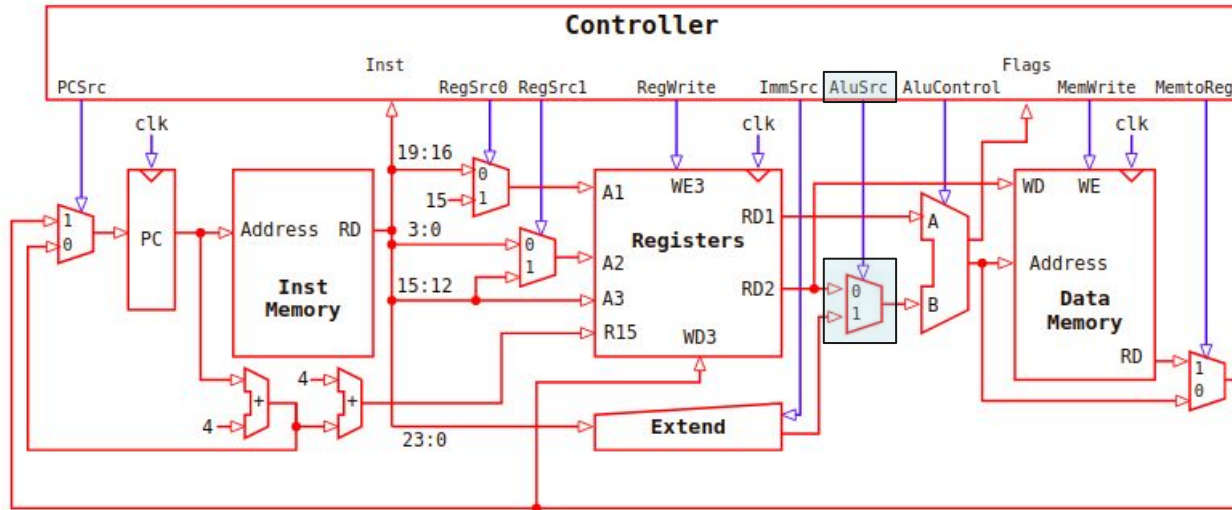- The data processing instructions using only register operands sets control to 0
- The memory, branch, and data (using immediate) instructions sets the control to 1




Control Lines - AluControl

- The controls are: ADD, SUB, AND, OR

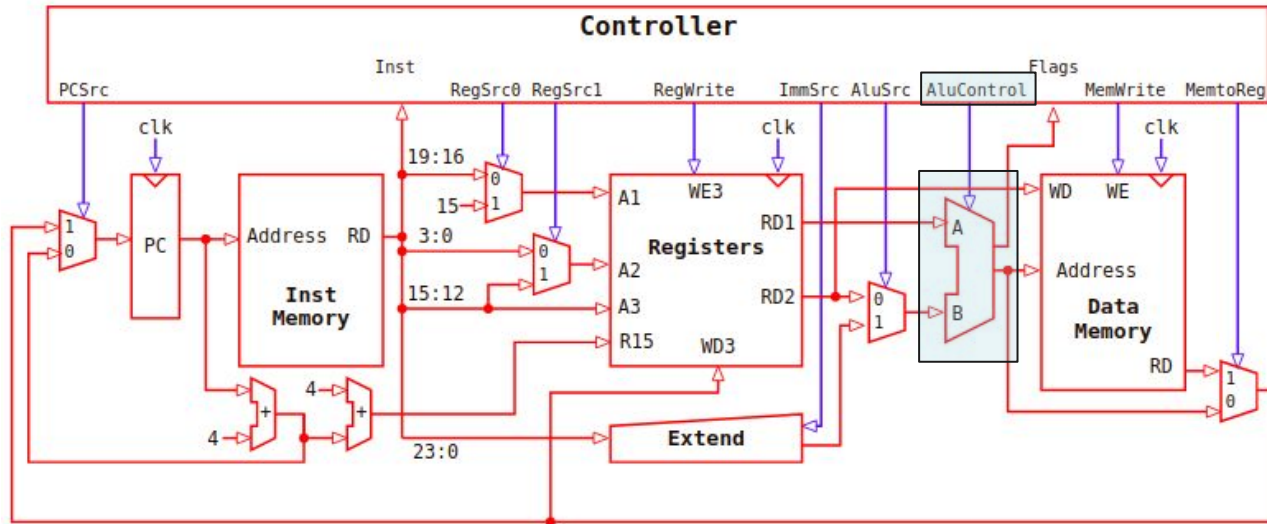


Control Lines - MemWrite

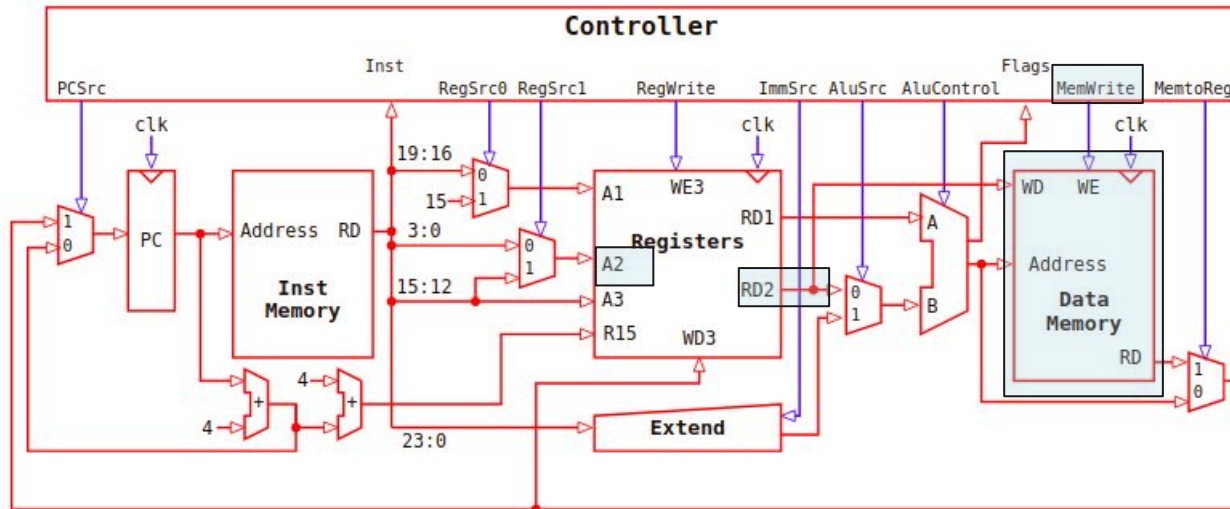- Memory is updated with MemWrite is 1, data (WD) comes from RD2, RegSrc1 = 1
 - otherwise memory is not updated
- The STR instruction will set MemWrite to 1
- This control is 0 if the result is not used.



Control Lines - MemtoReg

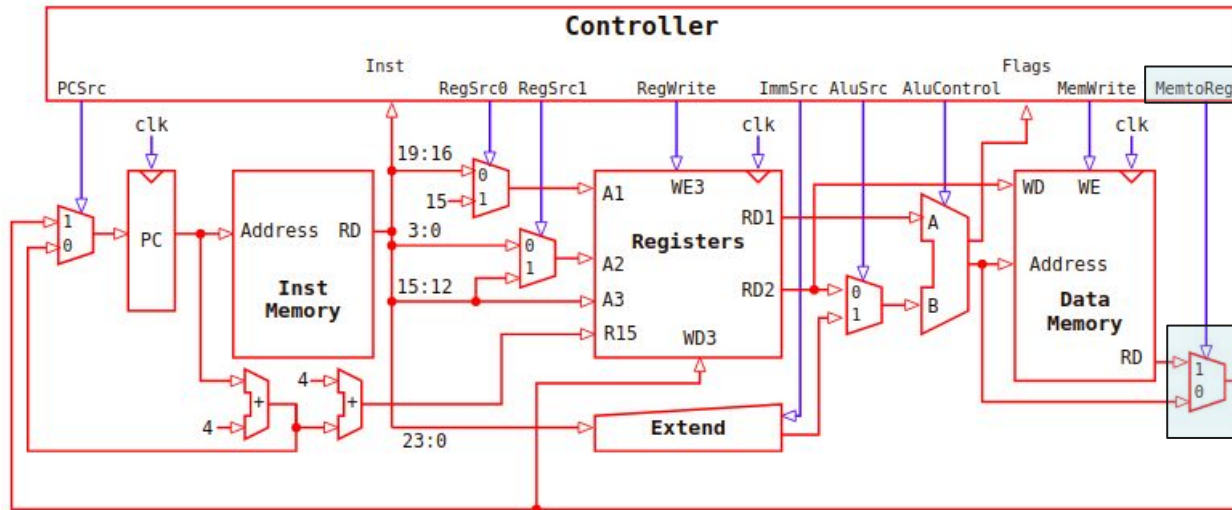
- This control selects between the data memory and the ALU
- MemtoReg is set to 1 for LDR instructions, 0 for Data instructions (store to register), and don't care for STR instructions.



ORR R2, R3, R4 (R2 <= R3 | R4)


(e1832004) 1110 00 0 1100 0 0011 0010 00000 00 0 0100

cond	Op	I	CMD	S	Rn	Rd	shamt5	sh	R	Rm
1110	00	0	1100	0	0011	0010	00000	00	0	0100
31:28	27:26		25:20		19:16	15:12	11:0			

 

ORR R2, R3, R4 (R2 <= R3 | R4)

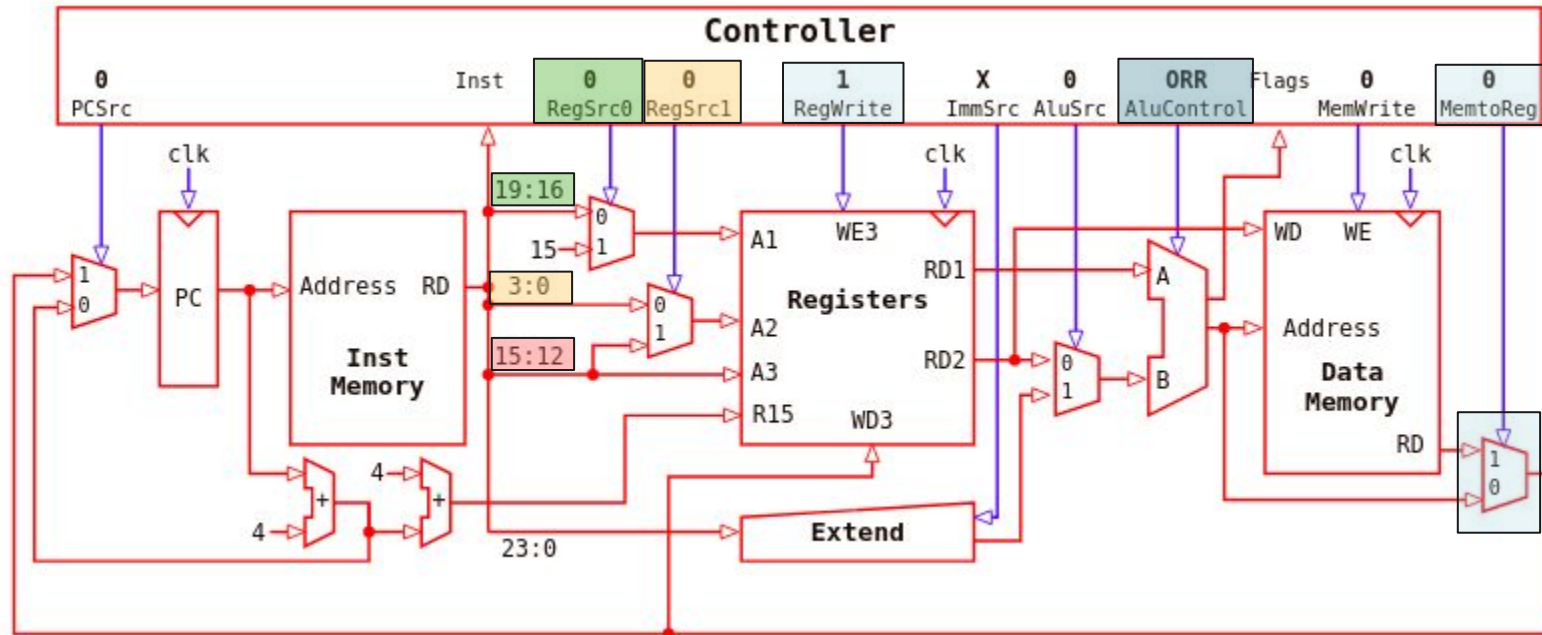(e1832004) 1110 00 0 1100 0 0011 0010 00000 00 0 0100



ORR R2, R3, R4 (R2 <= R3 | R4)




The rationale for these settings are:

- PCSrc=0 For all data processing instruction the next instruction (PC+4) is executed
- RegSrc0=0 The first source operand Rn is selected
- RegSrc1=0 The second source operand Rm is selected
- RegWrite=1 The result of ORR is stored, thus the register file is updated
- ImmSrc=X Since AluSrc=0 the output of the extend module is ignored
- AluSrc=0 Set to 0 to select data from the second register operand
- AluControl=ORR AluControl is ORR to OR the two registers
- MemWrite=0 The memory is not modified
- MemtoReg=0 The result from the ALU is sent to the register file

AND R3, R8, #15 (R3 <= R8 & 15) Immediate op [Left here]


(e208300f) 1110 00 1 0000 0 1000 0011 0000 00001111

cond	Op	I	CMD	S	Rn	Rd	rot	imm8
1110	00	1	0000	0	1000	0011	0000	00001111
31:28	27:26		25:20		19:16	15:12		11:0

 

AND R3, R8, #15 ($R3 \leftarrow R8 \& 15$) Immediate op

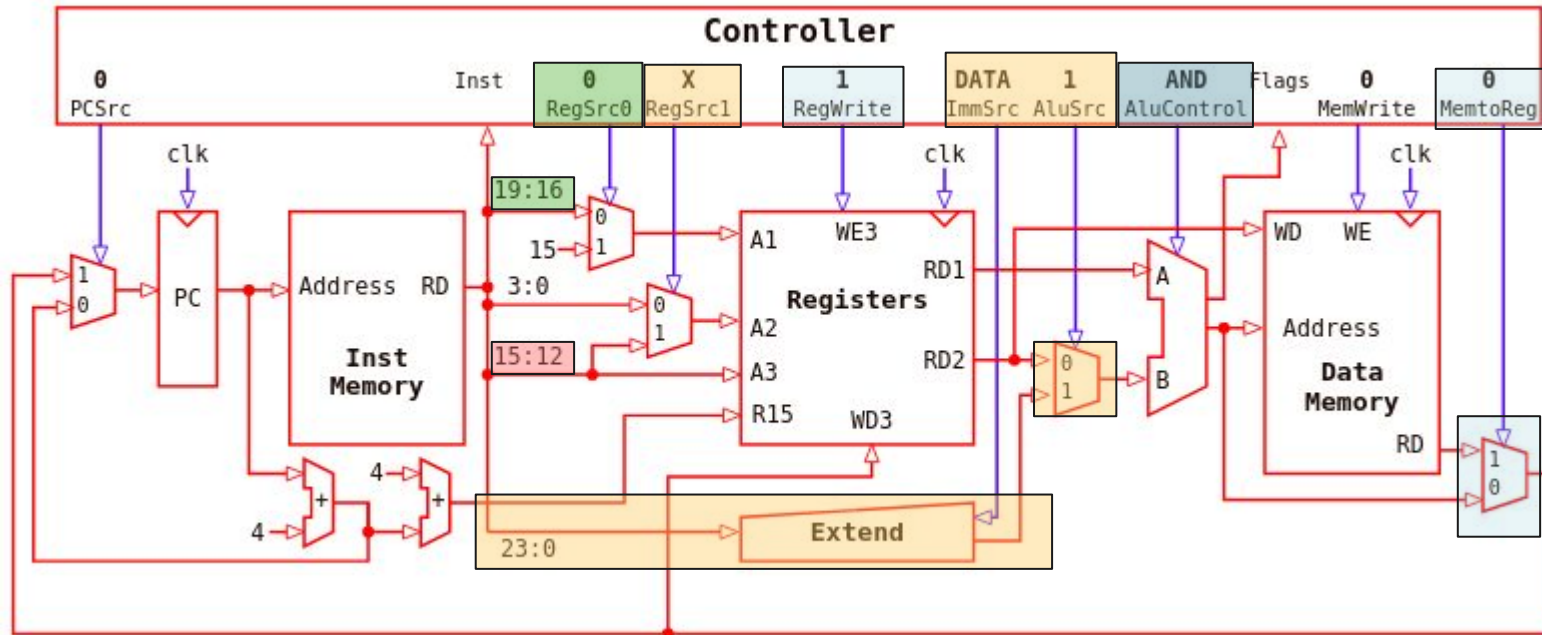(e208300f) 1110 00 1 0000 0 1000 0011 0000 00001111



AND R3, R8, #15 (R3 <= R8 & 15) Immediate op

Controller										
0	Inst	0	X	1	DATA	1	AND	Flags	0	0
PCSrc		RegSrc0	RegSrc1	RegWrite	ImmSrc	AluSrc	AluControl		MemWrite	MemtoReg

The rationale for these settings are:

- PCSrc=0 For all data processing instruction the next instruction (PC+4) is executed.
- RegSrc0=0 The first source operand Rn is selected.
- RegSrc1=X The second source operand Rm is ignored.
- RegWrite=1 The result of AND is stored, thus the register file is updated.
- ImmSrc=DATA The immediate data operand is used, this zero extends the lower 8 bits.
- AluSrc=1 Set to 1 to select data from the extend module.
- AluControl=AND AluControl is AND to AND the the operands.
- MemWrite=0 The memory is not modified.
- MemtoReg=0 The result from the ALU is sent to the register file.

LDR R1, [R2] (R1 <= M[R2])

Transfers the content of memory specified by R2 to the R1 register (memory operation)

(I=immed;

PW = 10 = offset; // all instructions will use offset


LB: STR = 00; STRB = 01; LDR = 10, LDRB = 11;

U=1=ADD // all instruction will use add)

(e5921000) 1110 01 011001 0010 0001 000000000000


cond	Op	\bar{I} PUBWL	Rn	Rd	Immd
1110	01	011001	0010	0001	000000000000
31:28	27:26	25:20	19:16	15:12	11:0

Memory

 

Frequency	Percentage
Never	10%
Sometimes	40%
Often	50%

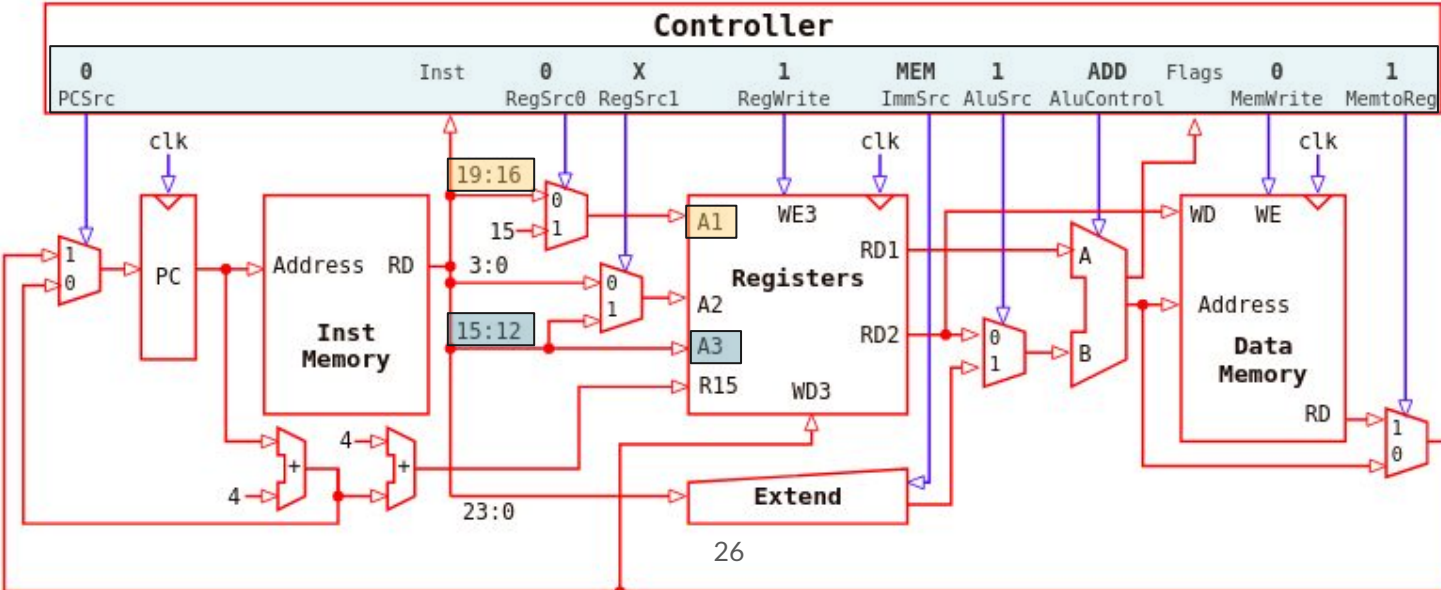(e5921000) 1110 01 011001 0010 0001 000000000000



LDR R1, [R2] (R1 <= M[R2])



The rationale for these settings are:


- PCSrc=0 In load instructions the next instruction will be executed; PC becomes PC+4
- RegSrc0=0 The Rn register is added to the immediate value to give the address of the location to read
- RegSrc1=X Since the read port 2 is not used by the LDR instruction; Rm not included
- RegWrite=1 The LDR instruction updates the register file, thus the control must be 1 to enable the write
- ImmSrc=MEM Selects bits 11:0 to calculate the address to be read; MEM op
 - These bits are zero extended
- AluSrc=1 Set to 1 to select data from the extend module
- AluControl=ADD AluControl is ADD to add the register and immediate value
- MemWrite=0 MemWrite is 0 to read data from the memory
- MemtoReg=1 MemtoReg is 1 to select data from the memory to send to the register file

LDR R1, [R2, #40] (R1 <= M[R2 + 40])

Transfers the content of memory specified by R2 plus 40 to the R1 register

(e5921028) 1110 01 01100 1 0010 0001 000000101000 (40 is 0x28)

cond	Op	\bar{I} PUBWL	Rn	Rd	Immd
1110	01	01100 1	0010	0001	000000101000
31:28	27:26	25:20	19:16	15:12	11:0

 

LDR R1, [R2, #40] ($R1 \leftarrow M[R2 + 40]$)

Transfers the content of memory specified by R2 plus 40 to the R1 register

(e5921028) 1110 01 011001 0010 0001 000000101000 (40 is 0x28)

cond	Op	̄IPUBWL	Rn	Rd	Immd
1110	01	011001	0010	0001	000000101000
31:28	27:26	25:20	19:16	15:12	11:0

In hardware the following are identical:

```
ldr r1, [r2]
```

```
ldr r1, [r2, #0]
```

The assembler uses the simpler syntax when the offset is 0


STR R1,[R2,#48] (M[R2 + 48] <= R1)

The STR instruction copies R1 in to the location specified by R2 plus 48

(I=immed; PW = 10 = offset; LB => STR = 00; STRB = 01; LDR = 10; LDRB = 11; U=1=ADD)

(e5821030) 1110 01 01100 0 0010 0001 000000110000


cond	Op	\bar{I} PUBWL	Rn	Rd	Immd
1110	01	01100 0	0010	0001	000000110000
31:28	27:26	25:20	19:16	15:12	11:0

 

STR R1,[R2,#48] ($M[R2 + 48] \leftarrow R1$)

The STR instruction copies R1 in to the location specified by R2 plus 48

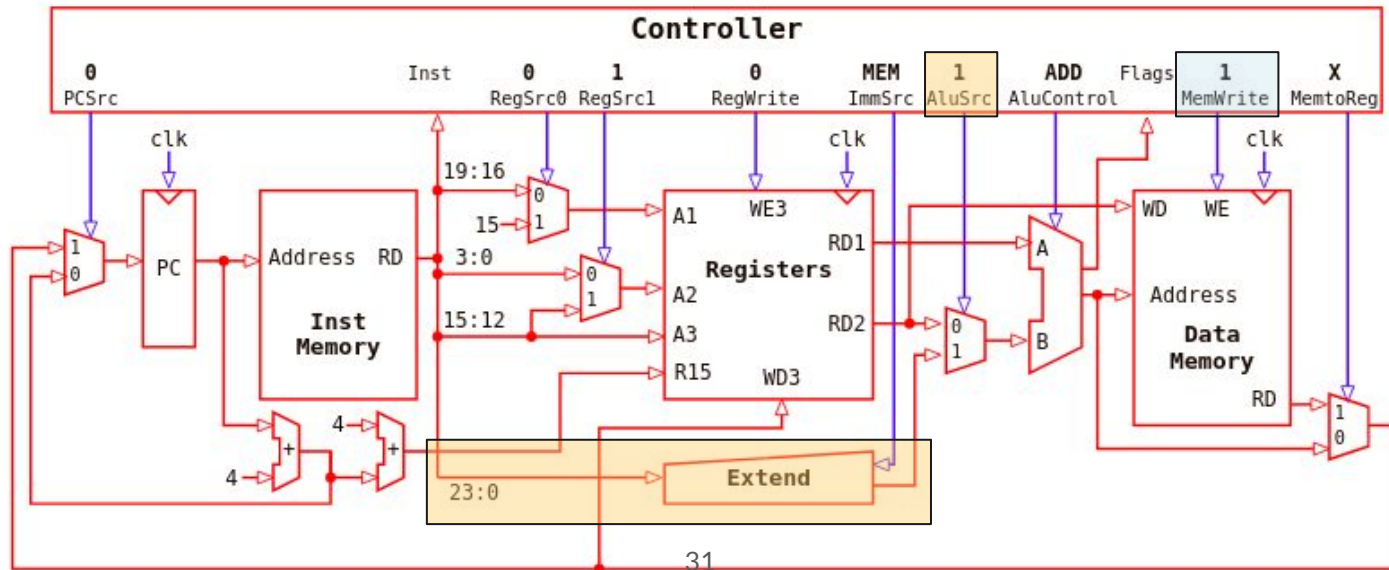(e5821030) 1110 11 011000 0010 0001 000000110000



STR R1,[R2,#48] (M[R2 + 48] <= R1)



The rationale for these settings are:

- PCSrc=0 In STR instructions the next instruction will be executed, so the PC becomes PC+4
- RegSrc0=0 The Rn register added to the immediate value to give the address of the location to read
- RegSrc1=1 Read port 2 outputs the register to be stored in memory; The register to store is specified in bits 15:12
- RegWrite=0 The register is not updated by the STR instruction
- ImmSrc=MEM Selects bits 11:0 to calculate the address to be read
- AluSrc=1 Set to 1 to select data from the extend module
- AluControl=ADD AluControl is ADD to add the register and immediate value
- MemWrite=1 MemWrite is 1 to write data to the memory
- MemtoReg=X MemtoReg is a don't care since the ALU result and data memory is not used


STR R1,[R2, R3, lsl #2] (M[R2 + R3 << 2] <= R1)

The STR instruction copies R1 in to the location specified by R2 plus R3 shifted by 2 (x4)

(Immediate $\tilde{I}=1$: shamt = 2 = 00010; sh = lsl = 00; RM = 3 = 0011)

(e5821030) 1110 01 111000 0010 0001 00010 00 1 0011

cond	Op	\tilde{I} PUBWL	Rn	Rd	Register
1110	01	111000	0010	0001	00010 00 1 0011
31:28	27:26	25:20	19:16	15:12	11:0

 

Branch instructions

Branches to an address that is N bytes ahead (N/4 words) funct = (B = always 1; L = 1 = BL, 0 = B)

The 24-bit immediate field gives the **number of instructions** between target and PC+8

The extended module multiply branch offset by 4.

Example ARM Assembly Code

```
0x80A0          B THERE                      // branch
0x80A4          ADDEQ R0, R1, R2             // PC+4
0x80A8          SUB R0, R0, R9               // PC+8
2 [ 0x80AC      ADD SP, SP, #8
    0x80B0 THERE SUB R0, R0, #1              //PC+8+(2 instructions)
    0x80B4      MOV PC, LR
    0x80B8      ADD R3, R3, #0x5
```

1011 10 10 0000 0000 0000 0000 0000 **0010**

immediate is **2** because target is three instructions past PC+8


B +2

Branches to an address that is 2 words/instructions ahead of PC+8 (16 bytes of PC)
 funct = (B = always = 1; L = 1 = BL, 0 = B)

(ea000002) 1110 10 10 00000000000000000000000010

cond	Op	1L	imm24
1110	10	10	00000000000000000000000010
31:28	27:26	25:24	23:0


Branch

 

B +2

Branches to an address that is 16 bytes ahead (PC + 8 + (2*4))

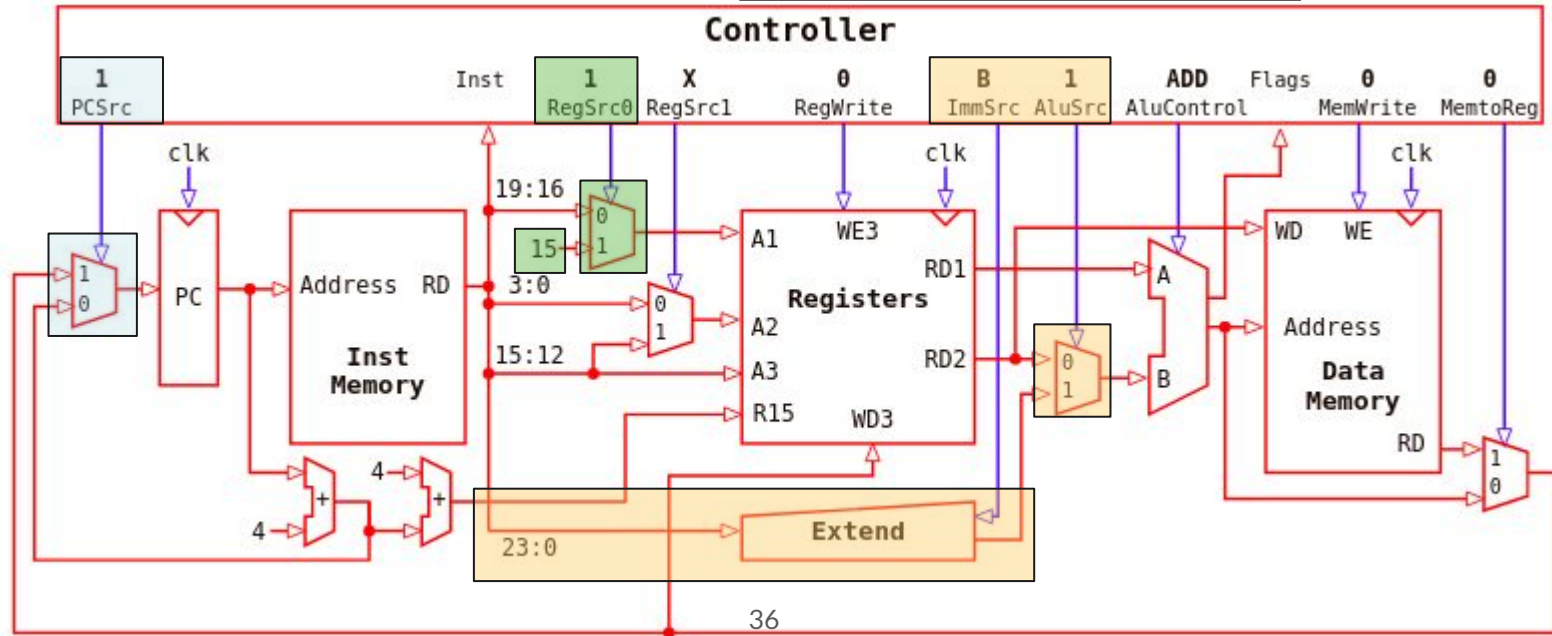(ea000002) 1110 10 10 00000000000000000000000010



B +2



The rationale for these settings are:

- PCSrc=1 The target of the branch address is sent to the PC.
- RegSrc0=1 The R15 (PC) is selected.
- RegSrc1=X The second source operand Rm is ignored.
- RegWrite=0 No registers are updated.
- ImmSrc=B The lower 23 bits are sign extended and multiplied by 4 to be added to the PC.
- AluSrc=1 Set to 1 to select data from the extend module.
- AluControl=ADD AluControl is ADD to add the the operands.
- MemWrite=0 The memory is not modified.
- MemtoReg=0 The result from the ALU is sent to the PC.

Recommended

- Review instructions format (Sections 6.4)
- Read section 7.3 textbook (Single-cycle Processor)



That's all folks

Final exam info soon