



Latches and Flip-flops



Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Combinational and Sequential Circuits

- Combinational logic
 - Output depends only on the current inputs
 - Truth table or boolean equation
- Sequential logic
 - Output depends on current and past inputs
 - Concept of the state
 - Current state analysis of the system to decide next state
 - Assembled to provide temporary memory
 - Discipline:
 - Block of combinational circuit;
 - with a bank of sequential circuit (Flip Flops) to keep the state.
 - Next lecture



Bi-stable Memory

  - Feedback is used to implement memory elements
 - Using two not gates to keep the same output/state
- Consider the following two NOT gates
- Output is feedback to the input
 - cross-coupled
- Same output until it has power




Bi-stable Memory

  - Has no inputs, no control over the behaviour
- When power is first applied
 - The initial state is unknown
 - Usually unpredictable
 - It may differ each time the circuit is turned on




SR Latch

 - The RS latch uses cross-coupled NOR gates
- NOR gate produces a FALSE output when either input is TRUE
- r stands for reset, and the s stands for set
- Two stable configurations



SR Latch

 - The RS latches uses cross-coupled NOR gates
- NOR gate produces a FALSE output when either input is TRUE
- r stands for reset, and the s stands for set
- Two stable configurations



```
1 module sr_latch(output logic q, nq,
2                 input logic s, r);
3     nor (q, r, nq);
4     nor (nq, s, q);
5 endmodule
```

S	R	Q	\bar{Q}
0	0	Latch	
0	1	0	1
1	0	1	0
1	1	Metastable	

SR Latch



```
module sr_latch(output logic q, n_q,  
input logic s, r);  
  
    nor nor_r(q, r, n_q);  
  
    nor nor_s(n_q, s, q);  
  
endmodule
```

```
`timescale 1ns/1ns
```


```
module main;  
    logic s, r;  
    logic q, n_q;  
  
    sr_latch dut(q, n_q, s, r);  
    initial begin  
        #10 $display("t=%04d sr q n_q", $time);  
        s = 0;  
        r = 0;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
        s = 0;  
        r = 1;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
        s = 1;  
        r = 0;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
        s = 0;  
        r = 1;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
        s = 0;  
        r = 0;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
        s = 0;  
        r = 0;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
        s = 1;  
        r = 1;  
        #10 $display("t=%04d %b%b %b %b", $time, s, r, q, n_q);  
    end  
endmodule
```

SR Latch

- sr_latch.vcd
- “Illegal” case

 
 


Case	S	R	Q	\bar{Q}
IV	0	0	Q_{prev}	\bar{Q}_{prev}
I	0	1	0	1
II	1	0	1	0
III	1	1	0	0

 


D-latch

  - The RS-latch can be modified to create a D-latch.
 - What should change
 - When it should change
- The D-latch (not gate) prevents illegal state.
- Sets in a specific time (clock)
 - Important for synchronous circuits



D-latch

 - If $CLK = 0$, both S and R are FALSE
 - regardless of the value of D.
 - Keep the last value
- If $CLK = 1$,
 - one AND gate will produce TRUE
 - the other FALSE
 - depending on the value of D
- Q is always the complement of \bar{Q}
- The D latch avoids the “illegal” case
 - $R=1, S=1$
- Challenge:
 - If D changes more than once during the clock=1



CLK	D	\bar{D}	S	R	Q	\bar{Q}
0	X	\bar{X}	0	0	Q_{prev}	\bar{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0

D-latch using gates


```
1 module d_latch_gate(output reg q, qbar,  
2                       input logic d, clk);  
3  
4     wire i_nand_q, i_nand_qbar, notd;  
5  
6     not(notd, d);  
7     and nandqb(i_nand_qbar, clk, d);  
8     and nandq(i_nand_q, clk, notd);  
9  
10    nor (q, i_nand_q, qbar);  
11    nor (qbar, i_nand_qbar, qbar);  
12  
13 endmodule
```

D-latch using behavioral verilog

```
1 module d_latch_behavior(output reg q, qbar,  
2                          input logic d, clk);  
3     always @(d, clk)  
4         if (clk) begin  
5             q <= d;  
6             qbar <= ~d;  
7         end  
8 endmodule
```

D-latch

 - tb_d_latch.vcd
- During one clock cycle you can have multiple values of d
 - multiple values of q and qbar




Flip-flops (D-FF)

- Synchronous circuits are designed to capture the input and change only with the clock changes.
- Rising edge or falling edge are used to sync the circuit.
- D-latches enable to changes during the clock cycle.
- Flip-flops avoid it

Flip-flops

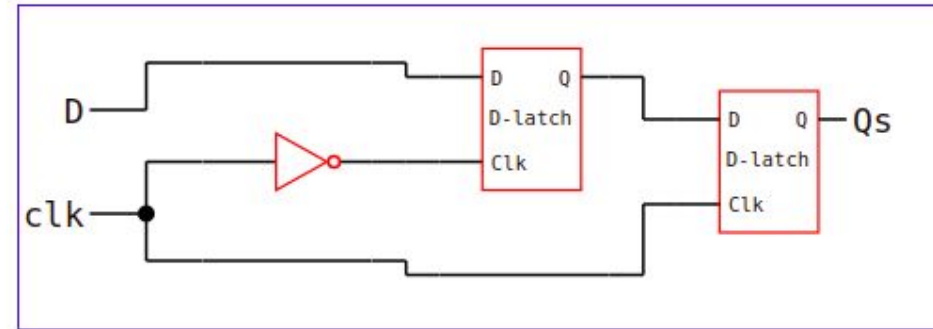- D-FF
- Back to back d-latches
- master/slave
- D flip-flop copies D to Q
- Rising edge of the clock
- Remembers its state at all other times



Flip-flops


- dff.vcd
- Only changes during the positive edge

```
1 module dff( output logic q, input logic d, clk);  
2     always_ff @(posedge clk) begin  
3         q <= #delay d;  
4     end  
5 endmodule
```




Enable Flip-flop

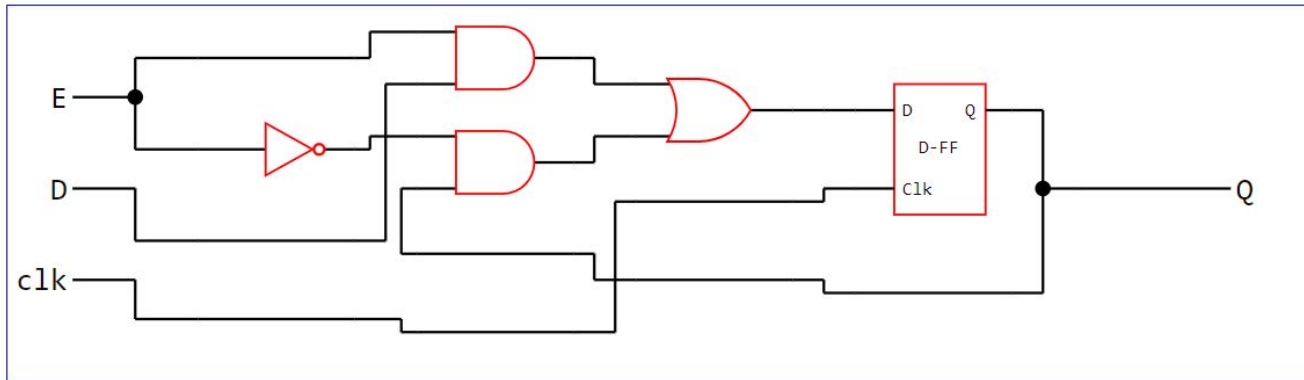- Extra ports are used to add functionality.
- It is important to control when the memory is invalid the system can disable the FF.
- Example in the notes
- Implementation in the next lab



Enable and Resettable Flip-flop

 - Extra ports are used to add functionality.
- It is important to control when the memory is invalid the system can reset or disable the FF.
- Example in the notes
- Implementation in the next lab



JK Flip Flop

- Not seen in this course
 - Versatile
 - Universal
 - Also has two set/reset inputs J and K
 - Inputs = 11, flips the value
 - Among other functionalities
- We will use the DFF for simplicity

Midterm material



The midterm cover topics seen in Units 1-3, from Lectures/slides 1-12 Latches and Flip-flops (included).



Questions?

- Next: 13 - Synchronous Sequential Circuits