

Controlling an ARM-like data path

Instructor: Dr. Vinicius Prado da Fonseca (vpradodafons@online.mun.ca)

Data path of arm-like


- This data path contains:
- 16-bit word 8 registers file with two read ports and one write port
 - `reg16_t R[7:0]; // registers`
- ALU with inputs a and b that supports
 - add
 - subtract
 - bitwise-or
 - bitwise-and
 - bitwise-xor
 - pass-b (output = operator b)
 - negate-b (invert signal)
 - invert-b (flip all bits)

```
typedef enum logic [2:0] {OP_ADD, OP_SUB, OP_ORR, OP_AND, OP_EOR, OP_B_NEG, OP_B_INV, OP_B_PAS} alu_ctl_t
```

- The shifter performs arithmetic right shift and logical left shift
 - `signed [4:0] shift_amt_t`

Data path of arm-like

- The block diagram is:

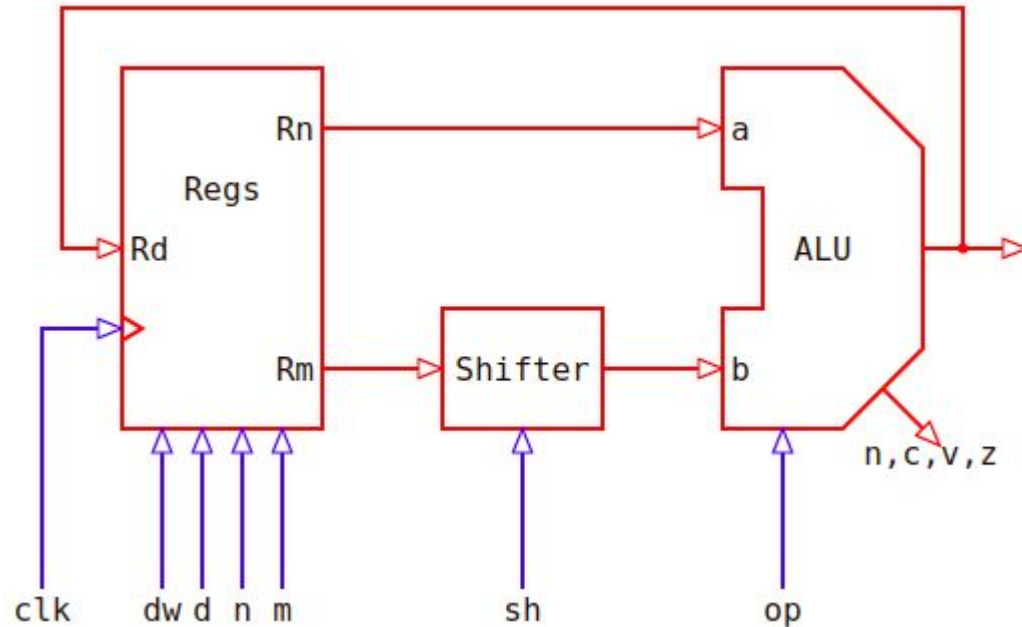


Data path of arm-like

- The data types for this data path are:

```
typedef logic [15:0] reg16_t;
typedef logic signed [4:0] shift_amt_t;
typedef logic [2:0] reg_sel_t;
typedef enum logic [2:0] {  OP_ADD, OP_SUB,
                             OP_ORR, OP_AND, OP_EOR,
                             OP_B_NEG, OP_B_INV, OP_B_PAS
                           } alu_ctl_t;
```

Data path of arm-like

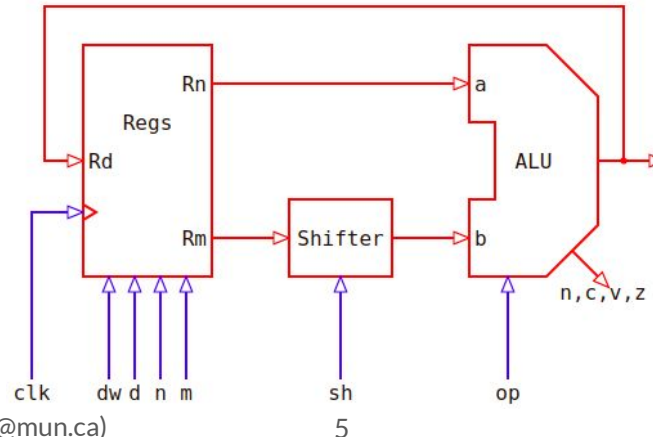
- armish_dp.v
- “shifter” module implements the combinational block that does right and left shift operations
- “arm_alu” implements the ALU
- The register file is implemented with reg_file
- The modules are combined to create the data path with the “armish_datapath” module



Data path of arm-like

The ports of the armish_datapath provide:

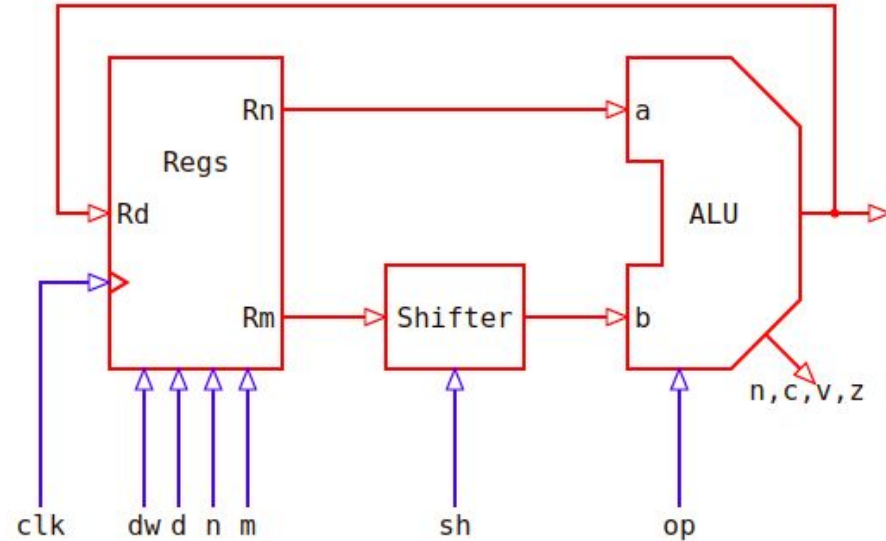
- outputs:
 - out - Output from the ALU (reg16_t)
 - cn - N (negative)
 - cz - Z (zero)
 - cc - C (carry out)
 - cv - V (overflow)
 - all operations set the flags
 - check the notes



Data path of arm-like

The ports of the armish_datapath provide:

- inputs:
 - op - specifies one of the operations (alu_ctl_t)
 - sh (signed) - controls the shift amount (shift_amt_t)
 - positive for left shifts
 - negative for arithmetic right shifts
 - d - selects the destination register that is updated (reg_sel_t)
 - n, m - register reading location
 - dw, clk, reset
 - dw enables register file updates. dw is 1, the output of the ALU is stored
 - clk is the clock signal for the positive edge flip-flops
 - reset clears all the flip-flops to zero.

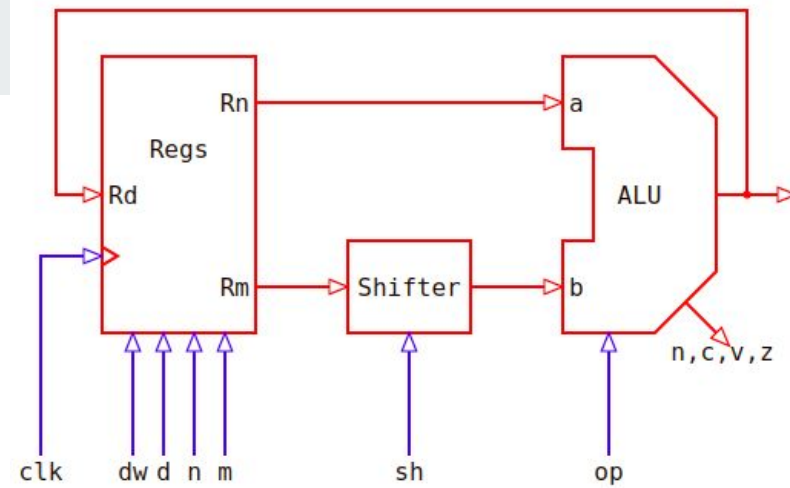


RTL Description of the data path

- The behaviour of this data path can be analysed at the register transfer level

$R[0] \leftarrow R[1] + R[5]$

$dw=?; d=?; n=?; m=?; sh=?; op=?$

 


dw	d	n	m	sh	op	RTL
1	x	-	z	0	pass_b	$R[x] \leftarrow R[z]$
1	x	-	z	0	invert_b	$R[x] \leftarrow \sim R[z]$
1	x	-	z	0	negate_b	$R[x] \leftarrow -R[z]$
1	x	y	z	0	or	$R[x] \leftarrow R[y] \mid R[z]$
1	x	y	z	0	eor	$R[x] \leftarrow R[y] \wedge R[z]$
1	x	y	z	0	and	$R[x] \leftarrow R[y] \& R[z]$
1	x	y	z	0	add	$R[x] \leftarrow R[y] + R[z]$
1	x	y	z	0	sub	$R[x] \leftarrow R[y] - R[z]$
0	-	y	z	0	sub	$R[y] - R[z]$ for compare
1	x	y	z	sh	op	$R[x] \leftarrow R[y] \text{ op } (R[z] \ll \text{sh})$ sh is positive
1	x	y	z	sh	op	$R[x] \leftarrow R[y] \text{ op } (R[z] \gg \text{sh})$ sh is negative

RTL Description of the data path

- The behaviour of this data path can be analysed at the register transfer level

$R[0] \leq R[1] + R[5]$

$dw=1; d=0; n=1; m=5; sh=0; op=OP_ADD$

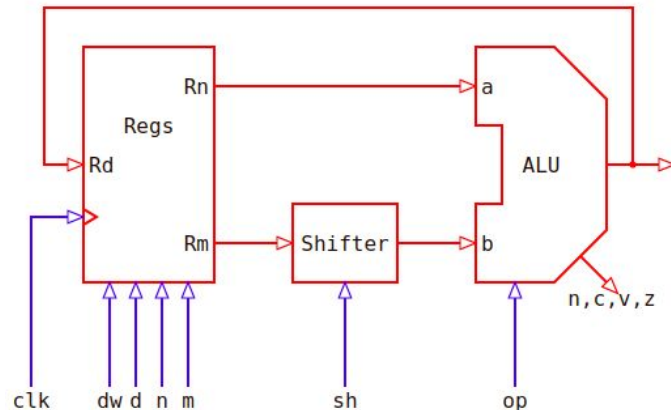

dw	d	n	m	sh	op	RTL
1	x	-	z	0	pass_b	$R[x] \leq R[z]$
1	x	-	z	0	invert_b	$R[x] \leq \sim R[z]$
1	x	-	z	0	negate_b	$R[x] \leq -R[z]$
1	x	y	z	0	or	$R[x] \leq R[y] \mid R[z]$
1	x	y	z	0	eor	$R[x] \leq R[y] \wedge R[z]$
1	x	y	z	0	and	$R[x] \leq R[y] \& R[z]$
1	x	y	z	0	add	$R[x] \leq R[y] + R[z]$
1	x	y	z	0	sub	$R[x] \leq R[y] - R[z]$
0	-	y	z	0	sub	$R[y] - R[z]$ for compare
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \ll \text{sh})$ sh is positive
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \gg \text{sh})$ sh is negative


RTL Description of the data path

- sh and alu in the same clock?

$R[1] \leq R[2] + R[5] \ll 1$

$R1 = R2 + R5 * 2$

dw=1; d=1; n=2; m=5; **sh=1**; op=OP_ADD

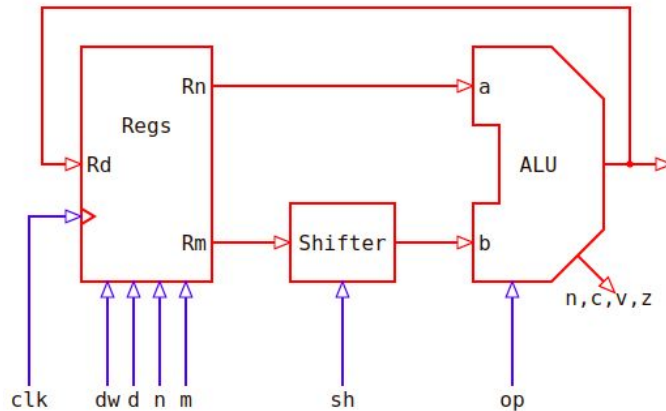

dw	d	n	m	sh	op	RTL
1	x	-	z	0	pass_b	$R[x] \leq R[z]$
1	x	-	z	0	invert_b	$R[x] \leq \sim R[z]$
1	x	-	z	0	negate_b	$R[x] \leq -R[z]$
1	x	y	z	0	or	$R[x] \leq R[y] \mid R[z]$
1	x	y	z	0	eor	$R[x] \leq R[y] \wedge R[z]$
1	x	y	z	0	and	$R[x] \leq R[y] \& R[z]$
1	x	y	z	0	add	$R[x] \leq R[y] + R[z]$
1	x	y	z	0	sub	$R[x] \leq R[y] - R[z]$
0	-	y	z	0	sub	$R[y] - R[z]$ for compare
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \ll \text{sh})$ sh is positive
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \gg -\text{sh})$ sh is negative


RTL Description of the data path

- Only shifting?

$R[1] \leq R[5] \ll 1$ (operand b, m)

$R1 = R5 * 2$

dw=1; d=1; n=x; m=5; sh=1; op=OP_PASS_B

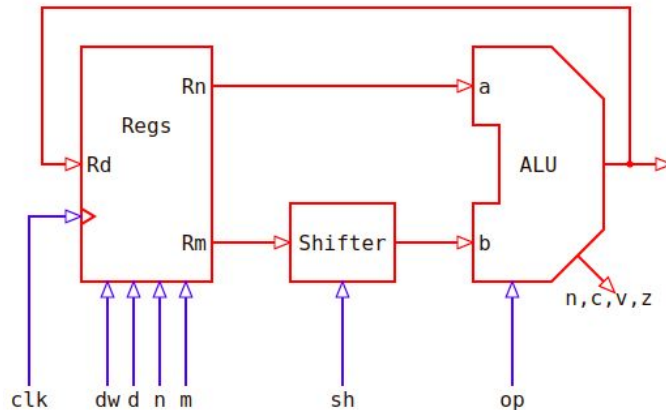


dw	d	n	m	sh	op	RTL
1	x	-	z	0	pass_b	$R[x] \leq R[z]$
1	x	-	z	0	invert_b	$R[x] \leq \sim R[z]$
1	x	-	z	0	negate_b	$R[x] \leq -R[z]$
1	x	y	z	0	or	$R[x] \leq R[y] \mid R[z]$
1	x	y	z	0	eor	$R[x] \leq R[y] \wedge R[z]$
1	x	y	z	0	and	$R[x] \leq R[y] \& R[z]$
1	x	y	z	0	add	$R[x] \leq R[y] + R[z]$
1	x	y	z	0	sub	$R[x] \leq R[y] - R[z]$
0	-	y	z	0	sub	$R[y] - R[z]$ for compare
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \ll \text{sh})$ sh is positive
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \gg \text{sh})$ sh is negative

RTL Description of the data path

- The behaviour of this data path can be analysed at the register transfer level
- sh and alu in the same clock

How to set **register 3** to 0?

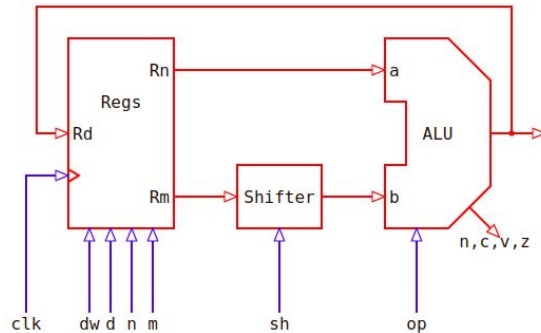



dw	d	n	m	sh	op	RTL
1	x	-	z	0	pass_b	$R[x] \leftarrow R[z]$
1	x	-	z	0	invert_b	$R[x] \leftarrow \sim R[z]$
1	x	-	z	0	negate_b	$R[x] \leftarrow -R[z]$
1	x	y	z	0	or	$R[x] \leftarrow R[y] \mid R[z]$
1	x	y	z	0	eor	$R[x] \leftarrow R[y] \wedge R[z]$
1	x	y	z	0	and	$R[x] \leftarrow R[y] \& R[z]$
1	x	y	z	0	add	$R[x] \leftarrow R[y] + R[z]$
1	x	y	z	0	sub	$R[x] \leftarrow R[y] - R[z]$
0	-	y	z	0	sub	$R[y] - R[z]$ for compare
1	x	y	z	sh	op	$R[x] \leftarrow R[y] \text{ op } (R[z] \ll \text{sh})$ sh is positive
1	x	y	z	sh	op	$R[x] \leftarrow R[y] \text{ op } (R[z] \gg -\text{sh})$ sh is negative

Controller for $R[3] \leftarrow 0$

- Register 3, $R[3]$, can be initialized to 0 with:

$S0: R[3] \leftarrow R[3] \wedge R[3]$

$op=OP_EOR, sh=0, d=3, n=3, m=3, dw=1$

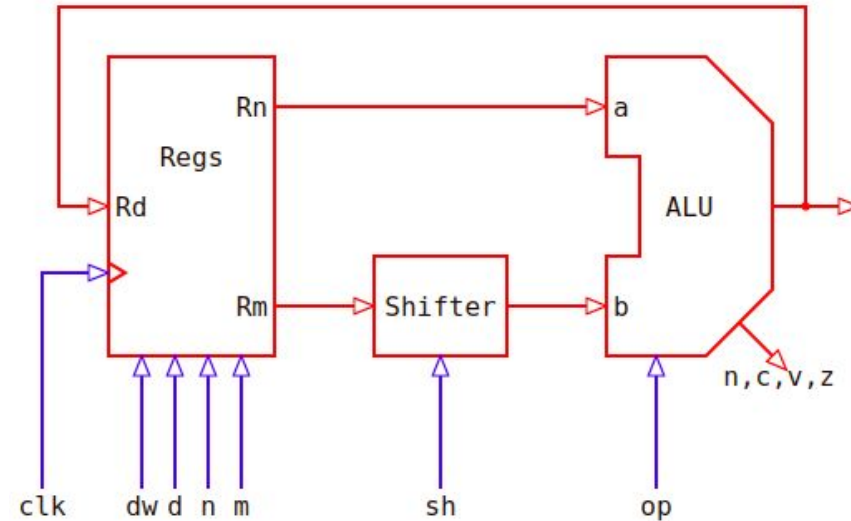 

Controller for $R[3] \leftarrow 0$



- Register 3, $R[3]$, can be initialized to 0 with:

S0: $R[3] \leftarrow R[3] \wedge R[3]$

op=OP_EOR, sh=0, d=3, n=3, m=3, dw=1

S1: pass_b($R[3]$)

op=OP_B_PAS, sh=0, d=0, n=0, m=3, dw=0

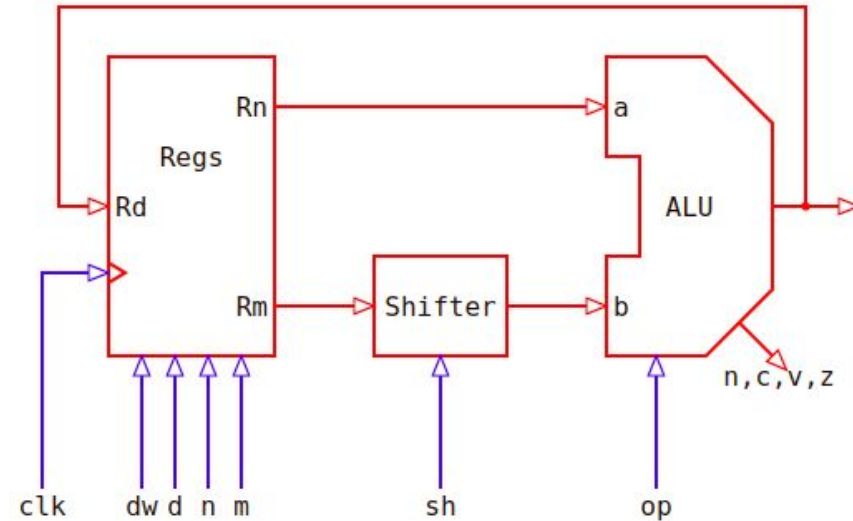 

Controller for $R[3] \leq 0$

- Register 3, $R[3]$, can be initialized to 0 with:


S0: $R[3] \leq R[3] \wedge R[3]$

op=OP_EOR, sh=0, d=3, n=3, m=3, dw=1

S1: pass_b($R[3]$)

op=OP_B_PAS, sh=0, d=0, n=0, m=3, dw=0

 
- S1 is used to output $R[3]$ through the ALU
- Transitions similar to mini datapath



Controller for R[6] <= 1


Register 6, R[6], can be initialized to 1 with:

dw	d	n	m	sh	op	RTL
1	x	-	z	0	pass_b	$R[x] \leq R[z]$
1	x	-	z	0	invert_b	$R[x] \leq \sim R[z]$
1	x	-	z	0	negate_b	$R[x] \leq -R[z]$
1	x	y	z	0	or	$R[x] \leq R[y] \mid R[z]$
1	x	y	z	0	eor	$R[x] \leq R[y] \wedge R[z]$
1	x	y	z	0	and	$R[x] \leq R[y] \& R[z]$
1	x	y	z	0	add	$R[x] \leq R[y] + R[z]$
1	x	y	z	0	sub	$R[x] \leq R[y] - R[z]$
0	-	y	z	0	sub	$R[y] - R[z]$ for compare
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \ll \text{sh})$ sh is positive
1	x	y	z	sh	op	$R[x] \leq R[y] \text{ op } (R[z] \gg -\text{sh})$ sh is negative

 

Controller for $R[6] \leq 1$

 
Register 6, $R[6]$, can be initialized to 1 with:



```
S0: R[6] <= R[6] ^ R[6]    // R[6] = 0000 0000 0000 0000
```

Controller for $R[6] \leq 1$

 Register 6, $R[6]$, can be initialized to 1 with:




S0: $R[6] \leq R[6] \wedge R[6]$ // $R[6] = 0000\ 0000\ 0000\ 0000$

S1: $R[6] \leq \sim R[6]$ // $R[6] = 1111\ 1111\ 1111\ 1111$

Controller for $R[6] \leq 1$

 Register 6, $R[6]$, can be initialized to 1 with:




S0: $R[6] \leq R[6] \wedge R[6]$ // $R[6] = 0000\ 0000\ 0000\ 0000$

S1: $R[6] \leq \sim R[6]$ // $R[6] = 1111\ 1111\ 1111\ 1111$

S2: $R[6] \leq R[6] \ll 1$ // $R[6] = 1111\ 1111\ 1111\ 1110$ (sh = 00001)

Controller for $R[6] \leq 1$

 Register 6, $R[6]$, can be initialized to 1 with:



S0: $R[6] \leq R[6] \wedge R[6]$ // $R[6] = 0000\ 0000\ 0000\ 0000$


S1: $R[6] \leq \sim R[6]$ // $R[6] = 1111\ 1111\ 1111\ 1111$

S2: $R[6] \leq R[6] \ll 1$ // $R[6] = 1111\ 1111\ 1111\ 1110$ (sh = 00001)

S3: $R[6] \leq \sim R[6]$ // $R[6] = 0000\ 0000\ 0000\ 0001$

Controller for $R[6] \leq 1$

 Register 6, $R[6]$, can be initialized to 1 with:



S0: $R[6] \leq R[6] \wedge R[6]$ // $R[6] = 0000\ 0000\ 0000\ 0000$

S1: $R[6] \leq \sim R[6]$ // $R[6] = 1111\ 1111\ 1111\ 1111$


S2: $R[6] \leq R[6] \ll 1$ // $R[6] = 1111\ 1111\ 1111\ 1110$ (sh = 00001)

S3: $R[6] \leq \sim R[6]$ // $R[6] = 0000\ 0000\ 0000\ 0001$

S4: `pass_b(R[6])`

Controller for $R[4] \leftarrow 32$ (hint: shifting)


$R[4]$ can be initialized to 32 with:

 

```
S0: R[4] <= R[4] ^ R[4]    // R[4] = 0000 0000 0000 0000
```

Controller for $R[4] \leq 32$

$R[4]$ can be initialized to 32 with:

 


S0: $R[4] \leq R[4] \wedge R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0000$

S1: $R[4] \leq \sim R[4]$ // $R[4] = 1111\ 1111\ 1111\ 1111$

Controller for $R[4] \leq 32$

$R[4]$ can be initialized to 32 with:

 


S0: $R[4] \leq R[4] \wedge R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0000$

S1: $R[4] \leq \sim R[4]$ // $R[4] = 1111\ 1111\ 1111\ 1111$

S2: $R[4] \leq R[4] \ll 1$ // $R[4] = 1111\ 1111\ 1111\ 1110$ (sh=00001)

Controller for $R[4] \leq 32$

$R[4]$ can be initialized to 32 with:

 

S0: $R[4] \leq R[4] \wedge R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0000$

S1: $R[4] \leq \sim R[4]$ // $R[4] = 1111\ 1111\ 1111\ 1111$

S2: $R[4] \leq R[4] \ll 1$ // $R[4] = 1111\ 1111\ 1111\ 1110$ (sh=00001)

S3: $R[4] \leq \sim R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0001$

Controller for $R[4] \leq 32$

$R[4]$ can be initialized to 32 with:



S0: $R[4] \leq R[4] \wedge R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0000$

S1: $R[4] \leq \sim R[4]$ // $R[4] = 1111\ 1111\ 1111\ 1111$

S2: $R[4] \leq R[4] \ll 1$ // $R[4] = 1111\ 1111\ 1111\ 1110$ (sh=00001)

S3: $R[4] \leq \sim R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0001$

S4: $R[4] \leq R[4] \ll 5$ // $R[4] = 0000\ 0000\ 0010\ 0000$ (sh=00101)

Controller for $R[4] \leq 32$

$R[4]$ can be initialized to 32 with:



S0: $R[4] \leq R[4] \wedge R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0000$

S1: $R[4] \leq \sim R[4]$ // $R[4] = 1111\ 1111\ 1111\ 1111$

S2: $R[4] \leq R[4] \ll 1$ // $R[4] = 1111\ 1111\ 1111\ 1110$ (sh=00001)

S3: $R[4] \leq \sim R[4]$ // $R[4] = 0000\ 0000\ 0000\ 0001$

S4: $R[4] \leq R[4] \ll 5$ // $R[4] = 0000\ 0000\ 0010\ 0000$ (sh=00101)

S5: `pass_b(R[4])`

- The first four states are, almost identical $R[6] = 1$

Controller for maximum of R[0], R[1], R[2]

A Python script that finds the maximum of r0, r1, and r2 is:

```
def max( r0, r1, r2):  
  
    if ( r0 < r1 ):  
  
        r0 = r1  
  
    if ( r0 < r2 ):  
  
        r0 = r2  
  
    return r0
```

Controller for maximum of R[0], R[1], R[2]

- A RTL description for finding maximum is:

```
S0: R[0] - R[1]           // compare R[0] and R[1] (OP_SUB, dw=0)
```

```
S1: R[0] <= R[1]         // R[1] is larger
```

```
S2: R[0] - R[2]           // compare R[0] and R[2] (OP_SUB, dw=0)
```

```
S3: R[0] <= R[2]         // R[2] is larger
```

```
S4: pass_b(R[0])         // output R[0]
```

- Transitions use cn (Negative) to skip states and perform the operation correctly

Controller for maximum of R[0], R[1], R[2]

```
case( st )
```

```
  S0: st <= cn ? S1 : S2;
```


```
  S1: st <= S2;
```

```
  S2: st <= cn ? S3 : S4;
```

```
  S3: st <= S4;
```

```
  S4: st <= S4;
```

```
endcase
```

 

Controller for summing n numbers

This controller is equivalent to the following Python script. Add numbers from n to zero.

```
n = 4    # R[0]


sum = 0  # R[2]

one = 1  # R[1]

while n > 0 :

    sum = sum + n

    n = n - one
```

 

Controller for summing n numbers


$R[0] = n$, $R[1] = 1$, and $R[2] = 0$

S0: $R[0] \mid R[0]$ // check if $R[0]$ is 0

S1: $R[2] \leq R[2] + R[0]$ // accumulate sum

S2: $R[0] \leq R[0] - R[1]$ // $n = n - 1$, check for 0

S3: `pass_b(R[2])` // output $R[2]$

 

Controller for summing n numbers


S0 and S2 go to the final state S3, if the data path's zero condition is true (cz = 1)

S0: st <= cz ? S3 : S1;

S1: st <= S2;

S2: st <= cz ? S3 : S1;

S3: st <= S3;

 

- Transitions use cz (Zero) to loop back to state S1 while R0 != 0

Controller for Euclid's algorithm

Euclid's algorithm is used to calculate the greatest common divisor

$a=12, b=4$

$12 > 4$

$a = 12 - 4, a = 8$

$8 > 4$

$a = 8 - 4, a = 4$

$a == b$, return 4

A Python's version is

```
def gcd( a, b) :  
    while a != b :  
        if a > b :  
            a = a-b  
        else :  
            b = b-a  
    return a
```

Controller for Euclid's algorithm

$R[3] = a$, and $R[4] = b$, an RTL implementation for Euclid's algorithm is:


```
S0: R[0] <= R[3] - R[4]          // check if a == b

S1: R[0] | R[0]                  // check if a-b is negative

S2: R[3] <= R[3] - R[4]          // a = a - b

S3: R[4] <= R[4] - R[3]          // b = b - a

 S4: pass_b(R[3])                 // output R[3]
```



Python:

```
def gcd( a, b ) :

    while a != b :

        if a > b :

            a = a-b

        else :

            b = b-a

    return a
```

Controller for Euclid's algorithm


S0: st <= cz ? S4 : S1; // a==b?

S1: st <= cn ? S3 : S2; // a<b?

S2: st <= S0;

S3: st <= S0;

S4: st <= S4;

 



Next steps

Examples in the notes

Run and modify the examples